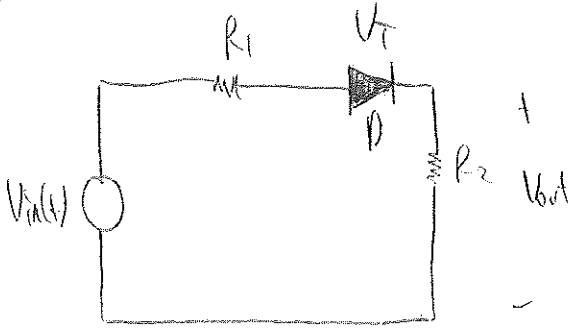


- Lab 2 -

3 a




$R_1 = R_2 = 10k\Omega$

$V_T = 0.7$  Volt (threshold voltage for the diode)


$V_{in} = 2 \sin(2\pi ft)$       $f = 10000 \text{ Hz}$

if  $V_{in}(t) > 0.7$      D is on  
 if  $V_{in}(t) < 0.7$      D is off  
 $V_{out}(t) = \frac{V_{in}(t) - 0.7}{10 + 10} \times 10$      when  $V_{in}(t) > 0.7$   
 $V_{out}(t) = 0$      when  $V_{in}(t) < 0.7$


$V_{in}(t)$  (Volt) [in DC mode]

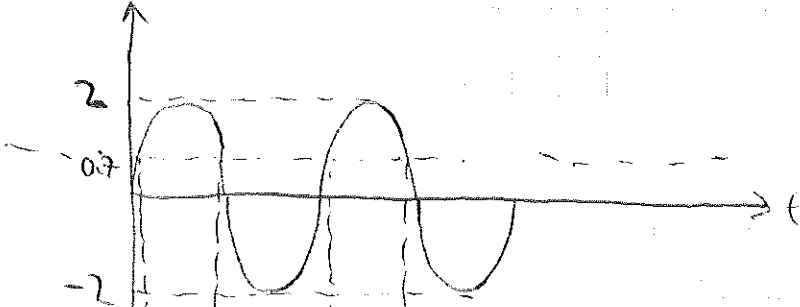

$V_{out}(t)$  (Volt) [in DC mode]

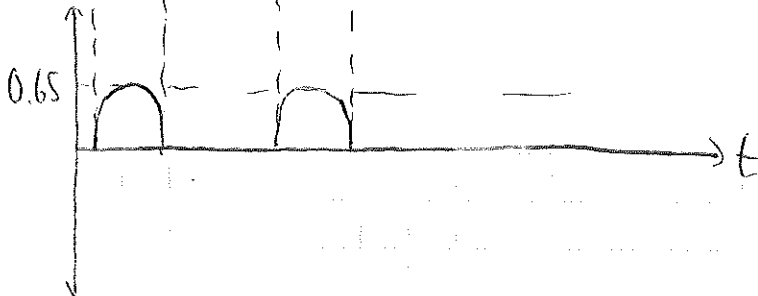

3 b

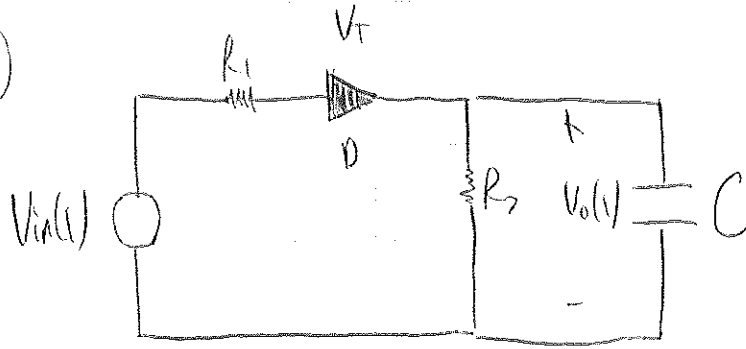

$$V_{in}(t) = 2 \sin(2\pi f t) \quad f = 10000 \text{ Hz}$$

$$R_1 = R_2 = 10 \text{ k}\Omega$$

$$C = 0.1 \text{ MF}$$


$$V_T = 0.7 \text{ Volt}$$

This is a rectifier circuit, it is used to obtain approximately DC Voltage from AC input.

① When the capacitor voltage increases  $V_{in} > V_T$  diode is on and the

② While the capacitor is discharged we have to compare the time constant of the  $R_2 C$  system with the period of the input. This happens when the diode is off


① When diode on

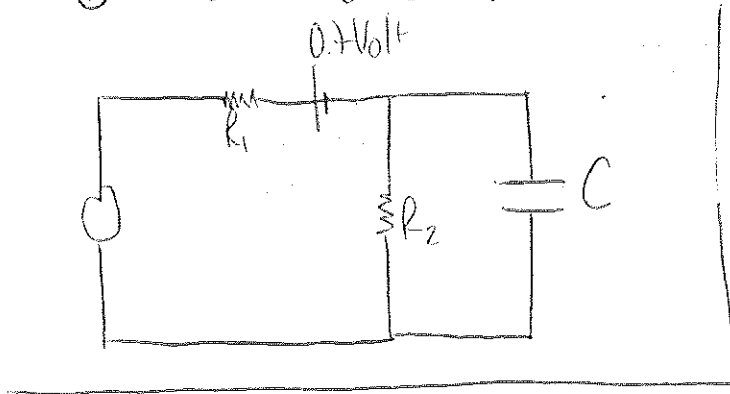

$$T = \frac{1}{f} = \frac{1}{10000} = 10^{-4} \text{ second}$$

period of input

② When diode off

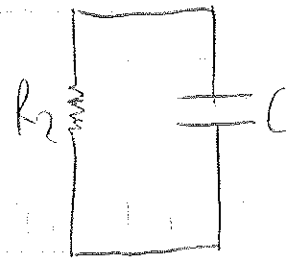

$$\tau = R_2 C = 10 \times 10^3 \times 0.1 \times 10^{-6}$$


$$= 1000 \times 10^{-7}$$

$$= 10^{-3} \text{ second}$$


time constant

$T \gg \tau$   
 (hence capacitor discharges very slowly compared to the change in input waveform)

$V_{out}(t) / V_{in}(t)$  in DC mode

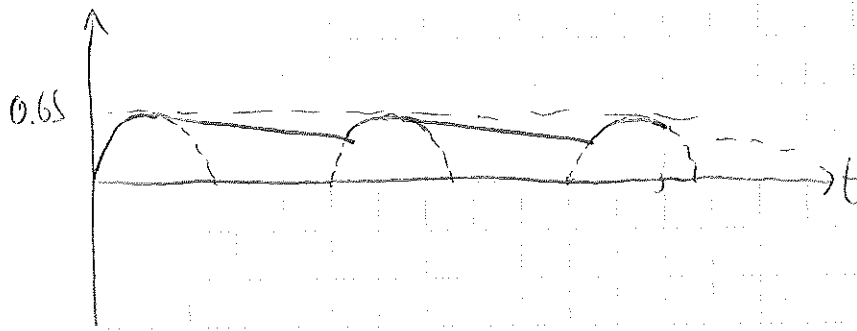

(3) (c)

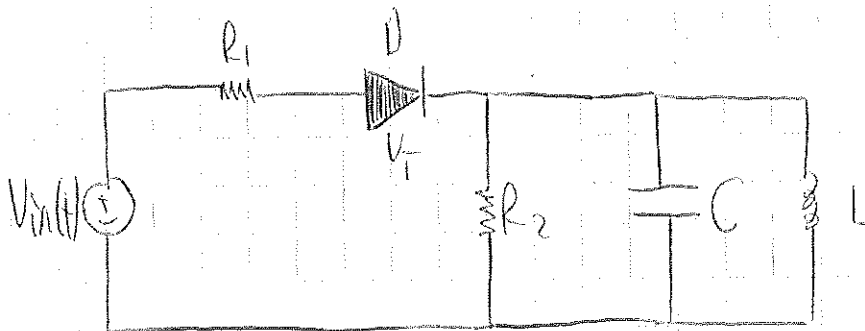


$R_1 = R_2 = 10 \Omega$

$C = 0.1 \mu F$     $L = 0.1 \text{ Henry}$

$V_{in}(t) = 2 \sin(2\pi f t)$

$f = 10000 \text{ Hz}$

use source transformation

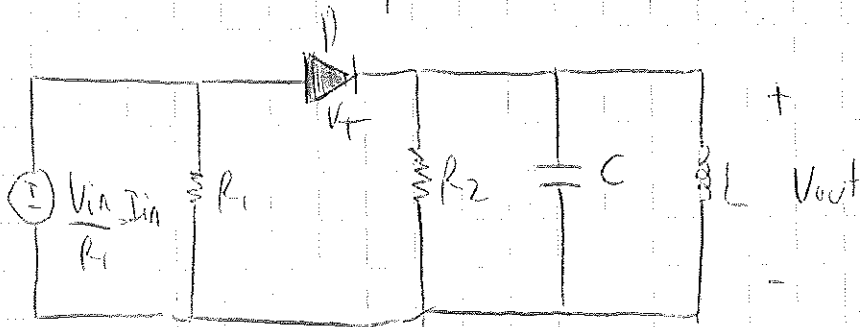

$I_{in} X(s) \approx V_{out}(s)$


[omitting the voltage drop over D] where diode is on

$\frac{V_{in}}{R_1} X(s) \approx V_{out}(s)$

where  $\frac{1}{X(s)} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{sC} + \frac{1}{sL}$

$\frac{V_{in}}{R_1} \frac{sLR_1R_2}{s^2LR_1R_2 + s[LR_2 + LR_1] + R_1R_2} \approx V_{out}(s)$

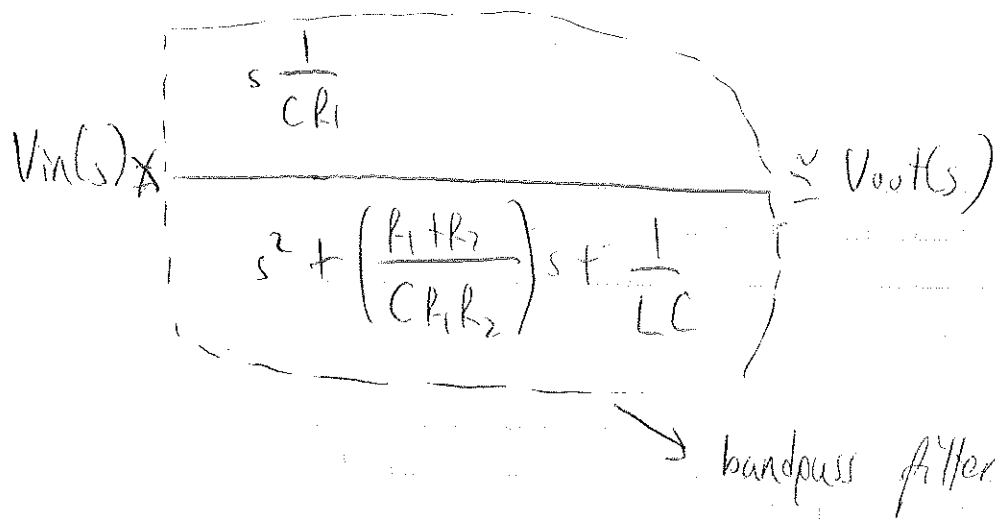$V_{in}(s) \frac{sLR_2}{s^2LR_1R_2 + s[LR_2 + LR_1] + R_1R_2} \approx V_{out}(s)$



maximum gain for bandpass filter is obtained

when  $\omega = \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.1 \times 0.1 \times 10^{-6}}} = \frac{1}{\sqrt{10^{-8}}} = 10000 \frac{\text{rad}}{\text{sec}}$

However  $V_{in}(t) = 2 \sin(2\pi f t)$  with  $f = 10000 \text{ Hz}$

$f_0 = \frac{\omega_0}{2\pi} = \frac{10000}{2\pi} \text{ Hertz}$

$f_0 \neq f$  [resonant frequency is not equal to input frequency]

\* Hence if  $V_{in}(t) = 2 \sin(2\pi f t)$  where  $f = 10000 \text{ Hz}$  the output will be composed of a very small portion of input signal, nearly no signal will be observed at the output