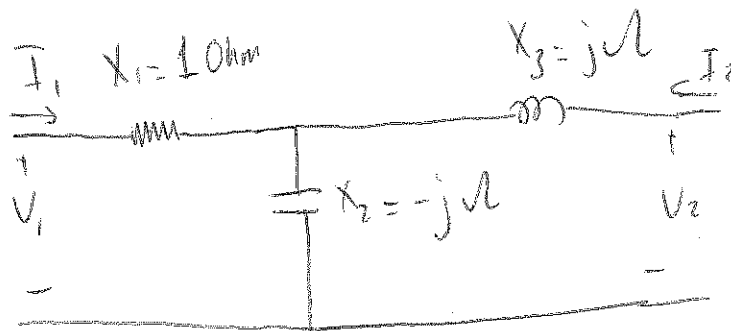


Q-1-



$$V_1 = X_1 I_1 + X_2 (I_1 + I_2)$$

$$V_1 = (X_1 + X_2) I_1 + X_2 I_2$$


$$V_2 = X_3 I_2 + X_2 (I_1 + I_2)$$

$$V_2 = X_2 I_1 + (X_2 + X_3) I_2$$

$$V_1 = (1-j) I_1 - j I_2 \quad V_2 = -j I_1 + 0 I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1-j & -j \\ -j & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Q-2

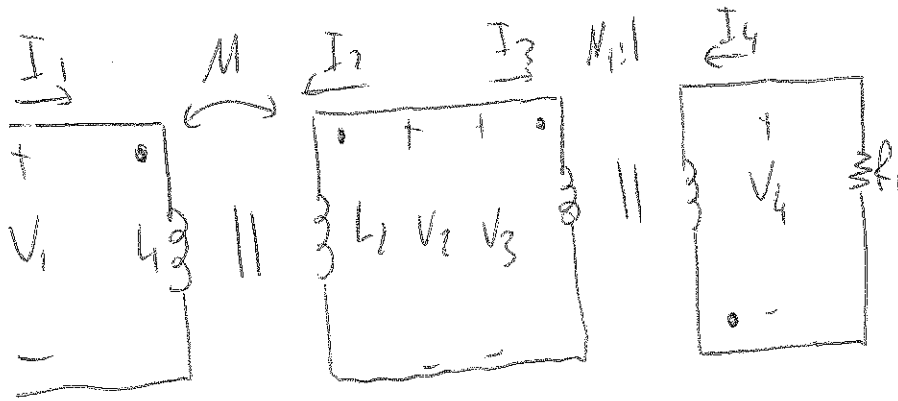

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} sL_1 & sM \\ sM & sL_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_3 = N_1 V_4$$

$$I_3 = \frac{1}{N_1} I_4$$

② $V_4 = -R_1 I_4$

② $V_2 = V_3$

② $I_3 = -I_4$

$$V_4 = -R_1 I_4 \rightarrow \frac{V_3}{-N_1} = -R_1 N_1 I_3 \quad V_3 = N_1^2 R_1 I_3 //$$

$$V_3 = V_2 = N_1^2 R_1 I_3 = -N_1^2 R_1 I_2 //$$

$$V_2 = sM I_1 + sL_2 I_2 \rightarrow -N_1^2 R_1 I_2 = sM I_1 + sL_2 I_2$$


$$0 = (N_1^2 R_1 + sL_2) I_2 + sM I_1 \quad I_2 = \frac{-sM}{N_1^2 R_1 + sL_2} I_1 //$$

$$V_1 = sL_1 I_1 + sM I_2 \quad V_1 = \left[sL_1 - \frac{s^2 M^2}{N_1^2 R_1 + sL_2} \right] I_1$$

$$Z_{in} = \frac{V_1}{I_1} = sL_1 - \frac{s^2 M^2}{N_1^2 R_1 + sL_2}$$

④

Q-3

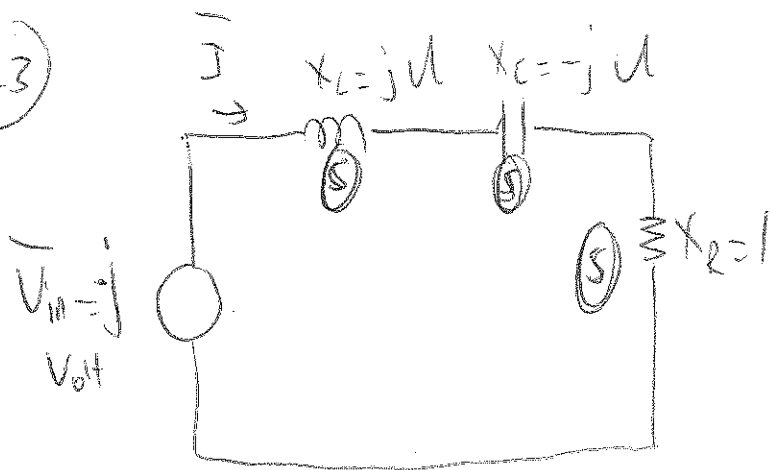


$$\sin(\omega t) \xrightarrow{\text{Phasor}} e^{-j90^\circ} = -j \quad (1)$$

$$\bar{I} = \frac{\bar{V}_{in}}{X_L + X_C + X_R} = \frac{j}{j + -j + 1} = j \text{ Ampere} \quad (1)$$

$$P_{X_R} = \frac{1}{2} \bar{I} \bar{I}^* R = \frac{1}{2} j \times j \times 1 = -\frac{1}{2} \text{ Watt} \quad (3)$$

Q-4

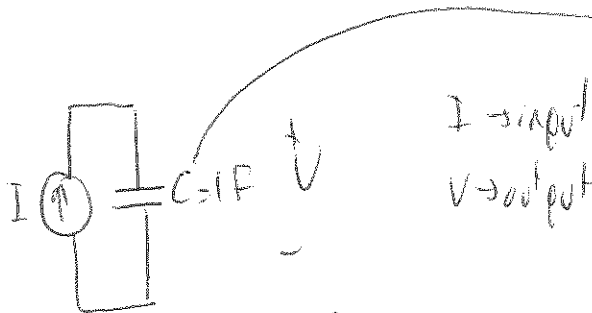

$$(5) \quad (a) \quad C \frac{dV}{dt} = I \xrightarrow{\mathcal{L}} CsV = I \quad \Rightarrow \frac{V}{I} = \frac{1}{sC} = \frac{1}{s} = H(s)$$

$$(5) \quad (b) \quad h(t) = \mathcal{L}^{-1} \left\{ \frac{1}{s} \right\} = u(t) \text{ (unit step function)}$$


$$(10) \quad (c) \quad \text{if } I(t) = u(t) \quad V(t) = \int_{-\infty}^t I(\tau) h(t-\tau) d\tau$$

$$V(t) = \int_{-\infty}^t u(\tau) u(t-\tau) d\tau = \int_0^t 1 \cdot 1 d\tau = \tau \Big|_0^t = t$$

$$V(t) = \begin{cases} 0, & t < 0 \\ t, & t > 0 \end{cases} \Rightarrow V(t) = |t|$$

↓ Volt
ramp function

Q5)

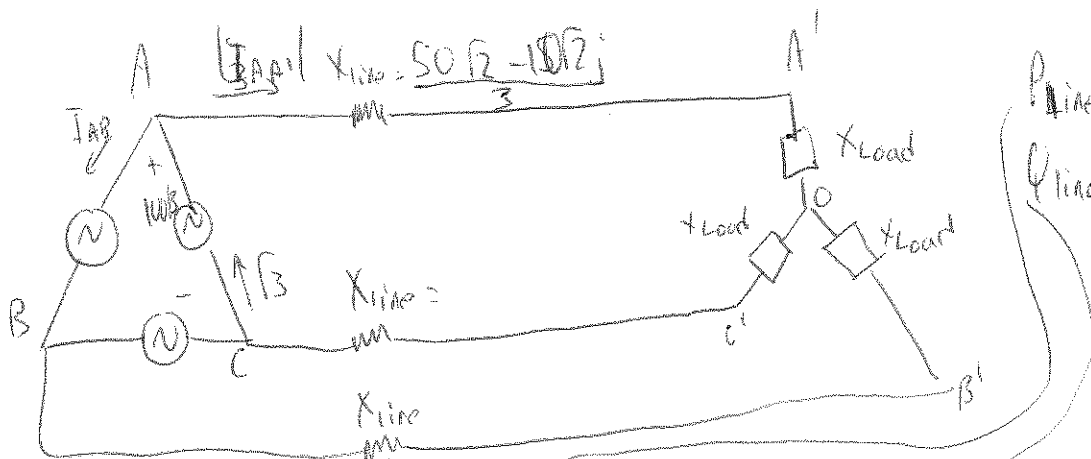

$$P_{line} = 3 + |I_{AA'}|^2 \times \text{Re}\{X_{line}\}$$

$$Q_{line} = 3 + |I_{AA'}|^2 \times \text{Im}\{X_{line}\}$$

(3)

(a)

$$|V_{AB}| = 100\sqrt{3} \text{ Volt (rms)}$$

$$Q_{source} = 450\sqrt{3} \text{ VAR}$$

$$P_{source} = 60\sqrt{3} \text{ Watt}$$

$$S_{source} = \sqrt{P_{source}^2 + Q_{source}^2}$$

$$|S_{source}| = 900 \text{ VA}$$

$$P_{line} = 3 + 3 + \frac{50\sqrt{3}}{3} \text{ Watt}$$

$$= 450\sqrt{3} \text{ Watt}$$

$$Q_{line} = 3 + 3(-100\sqrt{3})$$

$$= -90\sqrt{3} \text{ VAR}$$

$$P_{load} = P_{source} - P_{line}$$

$$= 0 \text{ Watt}$$

$$Q_{load} = Q_{source} - Q_{line}$$

$$= 450\sqrt{3} - (-90\sqrt{3})$$

$$= 560\sqrt{3} \text{ VAR}$$

$$|S_{load}| = \sqrt{P_{load}^2 + Q_{load}^2}$$

$$= 560\sqrt{3} \text{ VA}$$

(3)

$$|S_{source}| \Rightarrow |V_{AB}| / |I_{AB}| = 900 = 3 \times 100\sqrt{3} \times |I_{AB}|$$

$$|I_{AB}| = \sqrt{3} \text{ Ampere (rms)} \quad (3)$$

$$|I_{AA'}| = \sqrt{3} |I_{AB}| = 3 \text{ Ampere (rms)} \quad (3)$$

$$|S_{load}| = \sqrt{3} |V_{A'B'}| / |I_{AA'}|$$

$$|V_{A'B'}| = \frac{180\sqrt{3}}{\sqrt{3}} \text{ Volt (rms)}$$

$$560\sqrt{3} = \sqrt{3} |V_{A'B'}| \times 3$$

$$|V_{A'O}| = \frac{|V_{A'B'}|}{\sqrt{3}} = 60\sqrt{3} \text{ Volt (rms)}$$

$$X_{Load} = \frac{|V_{A'O}|}{|I_{AA'}|} = \frac{60\sqrt{3}}{3} = 20\sqrt{3} \Omega \quad (3)$$

$$S_{load} = P_{load} + jQ_{load} = -j560\sqrt{3} \text{ VA} \quad (1)$$

Since $Q_{load} < 0$ the load x is capacitive