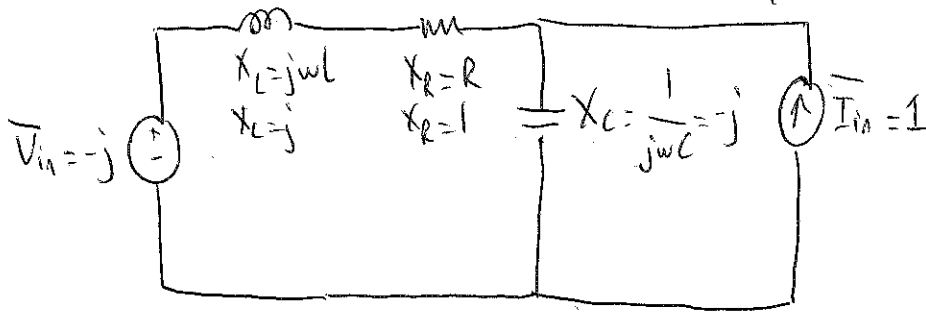


2013-2014


ECE 232 Midterm solutions

Q-1- In phasor domain $V_{in}(t) = \sin(\omega t) = \cos(\omega t - 90^\circ) \xrightarrow{\text{phasor}} \bar{V}_{in} = e^{-j90^\circ} = -j \text{ Volt}$
 $I_{in}(t) = \cos(\omega t) \text{ Ampere} \xrightarrow{\text{phasor}} \bar{I}_{in} = 1 \text{ Ampere}$



$X_L = j \cdot 1 \cdot 1 = j \checkmark$
 $X_C = \frac{1}{j\omega \cdot C} = \frac{1}{j} = -j \checkmark$
 $X_R = R = 1 \checkmark$

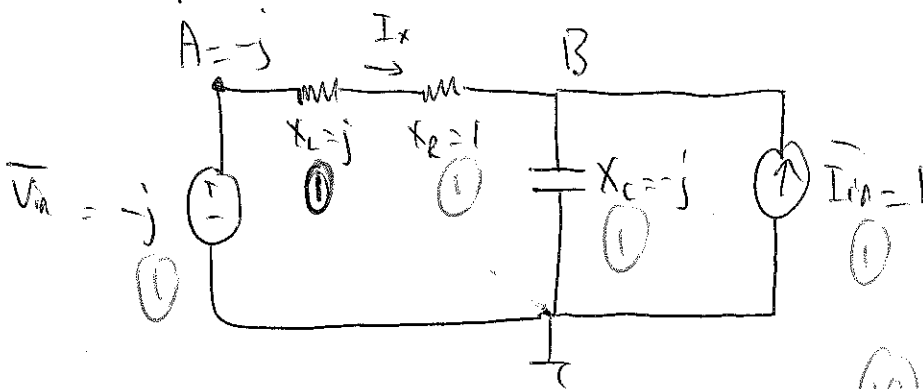Both for $V_{in}(t)$ and $I_{in}(t)$ $\omega = 1 \frac{\text{rad}}{\text{sec}}$



$$\frac{A-B}{X_L + X_R} + \bar{I}_{in} = \frac{B}{X_C}$$

$$\frac{-j - B}{j + 1} + 1 = \frac{B}{-j} \quad B = -j$$

$$I_x = \frac{A-B}{j+1} = \frac{-j - (-j)}{j+1} = 0$$

$$P_R = \frac{1}{2} I_x I_x^* R = \frac{1}{2} 0 \cdot 0 \cdot 1 = 0 \text{ Watt}$$



LILAS BELDEK

Q-2- $V_{in}(t) = \sin(t)$ Volt $\omega_1 = 1 \frac{\text{rad}}{\text{sec}}$ $I_{in}(t) = \cos(2t)$ Ampere $\omega_2 = 2 \frac{\text{rad}}{\text{sec}}$

The angular frequencies of the sources are different
 $\omega_1 \neq \omega_2$

Kill $V_{in}(t)$ (short circuit)

(1) → device self

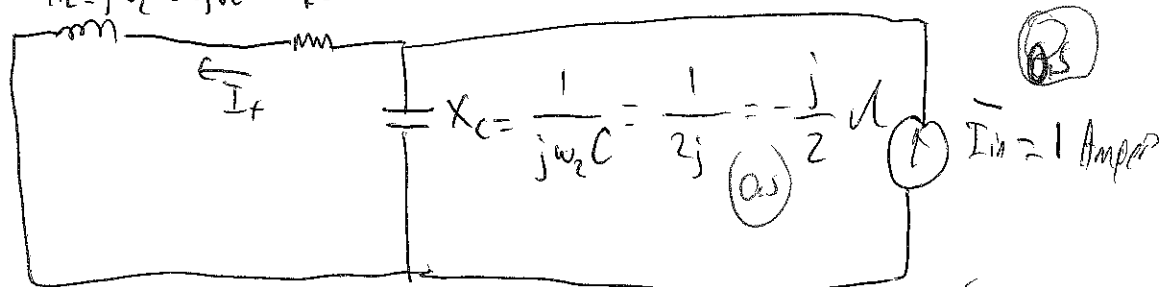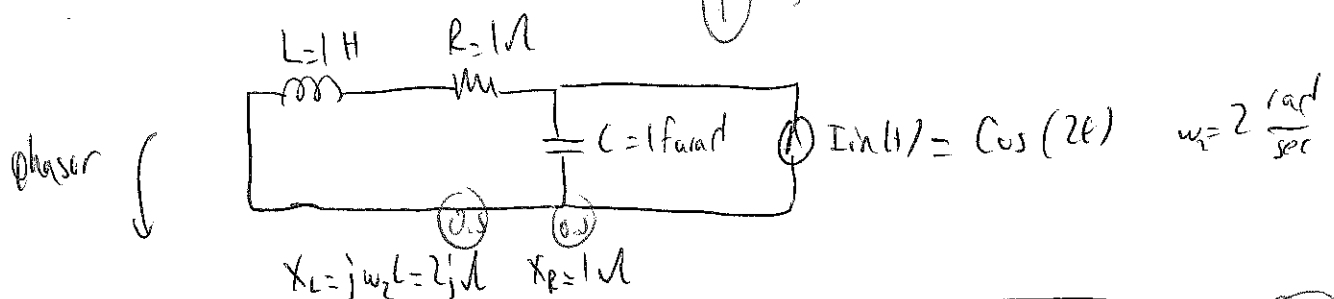

$$I_f = I_{in} \times \frac{X_C}{X_L + X_R + X_C} = 1 \times \frac{-\frac{j}{2}}{2j + 1 - \frac{j}{2}} = \frac{-\frac{j}{2}}{1 + \frac{3}{2}j} = \frac{-j}{2 + 3j} \quad (4)$$

$$I_f = -\frac{(2+3j)}{13} \text{ Ampere}$$


(1)

$$P_{L,R} = \frac{1}{2} I_f I_f^* R = \frac{1}{2} \left(\frac{2+3j}{13} \right) \left(\frac{2-3j}{13} \right) \times 1$$

$$= \frac{13}{2+13+13} = \frac{1}{26} \text{ Watt}$$

(2)

Killian Iin(t) (oper circuit)

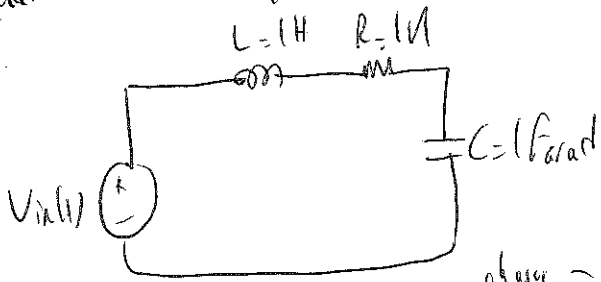


(1) → device setti

phasor $V_{in}(t) = \sin(t)$ Volt $\xrightarrow{\text{phasor}} \bar{V}_{in} = -j$ Volt

$\omega_1 = 1 \frac{\text{rad}}{\text{sec}}$

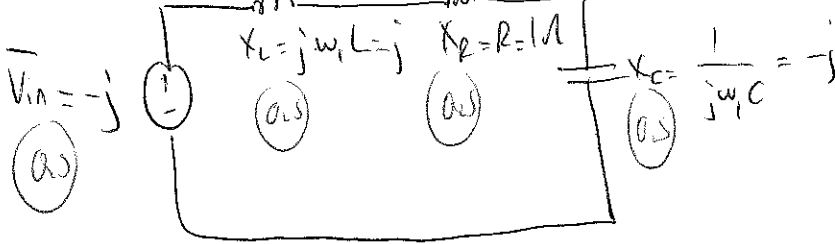$X_L = j\omega_1 L = j \Omega$
 $X_C = \frac{1}{j\omega_1 C} = -j \Omega$



$$I_y = \frac{\bar{V}_{in}}{X_L + X_R + X_C} = \frac{-j}{j + (j) + 1} = -j \quad (4)$$

(2)


$$P_{2,R} = \frac{1}{2} I_y I_y^* R = \frac{1}{2} \cdot (-j)(j) \cdot 1 = \frac{1}{2} \text{ Watt}$$

$$P_R = P_{1,R} + P_{2,R} = \frac{1}{26} + \frac{1}{2} = \frac{14}{26} \text{ Watt (average power over } R)$$

(2)

Q-3-

$R=1 \Omega$ $C=1 \text{ Farad}$

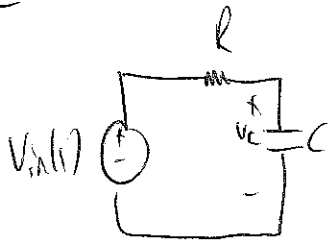

$$RC \frac{dv_c}{dt} + v_c = v_{in}$$

$$\frac{dv_c}{dt} + v_c = v_{in} \quad (2)$$

$$\frac{dv_c}{dt} + v_c = \sin(t)$$

$$\xrightarrow{\text{Laplace}} sV_c(s) - \underbrace{V_c(0)}_{1 \text{ Volt}} + V_c(s) = \frac{1}{s^2+1} \quad (5)$$

$$(s+1)V_c(s) = \frac{1}{s^2+1} + 1$$

$$V_c(s) = \frac{1}{(s+1)(s^2+1)} + \frac{1}{s+1} \quad (3)$$

$$V_c(s) = \frac{A}{s+1} + \frac{Bs+C}{s^2+1} + \frac{1}{s+1}$$

$$\left(\frac{A}{s+1} + \frac{Bs+C}{s^2+1} \right) = \frac{1}{(s+1)(s^2+1)} \quad (5)$$

$$A(s^2+1) + (Bs+C)(s+1) = 1$$

$$(A+B)s^2 + (B+C)s + (A+C) = 1$$

$$A = -B \quad B = -C \quad A+C = 1$$

$$A = C = \frac{1}{2} \quad B = -\frac{1}{2}$$

\mathcal{L}^{-1}

$$V_c(s) = \frac{1}{2} \frac{1}{s+1} + \frac{1}{2} \frac{s}{s^2+1} + \frac{1}{2} \frac{1}{s^2+1} + \frac{1}{s+1}$$

$$V_c(t) = \frac{1}{2} e^{-t} u(t) - \frac{1}{2} \cos(t) u(t) + \frac{1}{2} \sin(t) u(t) + e^{-t} u(t)$$

$$V_c(t) = \frac{3}{2} e^{-t} u(t) - \frac{1}{2} \cos(t) u(t) + \frac{1}{2} \sin(t) u(t)$$

Q-4 $H(s) = \frac{1000s}{(s+500)^2}$

(2) (a) $H(j\omega) = \frac{1000j\omega}{(j\omega+500)^2} = \frac{1000j\omega}{500^2 - \omega^2 + 1000j\omega}$

(2) (b) $|H(j\omega)| = \frac{1000\omega}{\omega^2 + 500^2}$ or $|H(j\omega)| = \frac{1000\omega}{\sqrt{(500^2 - \omega^2)^2 + (1000\omega)^2}}$

(2) (c) $\angle H(j\omega) = 90 - 2 \tan^{-1} \frac{\omega}{500}$

(2) (d) $|H(j\omega)|_{dB} = 20 \log \frac{1000\omega}{\omega^2 + 500^2}$

(3) (i) At the resonant frequency $|H(j\omega)|$ is maximized $\left(\frac{d|H(j\omega)|}{d\omega} \Big|_{\omega_{res}} = 0 \right)$

$$\frac{d}{d\omega} |H(j\omega)| = 1000 \left[\frac{1(\omega^2 + 500^2) - 2\omega(\omega)}{(\omega^2 + 500^2)^2} \right]$$

$$= \frac{1000}{\omega^2 + 500^2} [500^2 - \omega^2] \quad (2.5)$$

$$\frac{d}{d\omega} |H(j\omega)| \Big|_{\omega=\omega_{res}} = 0 \Rightarrow \frac{1000}{\omega_{res}^2 + 500^2} [500^2 - \omega_{res}^2] = 0$$

$$\omega_{res} = 500 \frac{\text{rad}}{\text{sec}} \quad (0.1)$$

$$|H(j\omega)| \Big|_{\omega=\omega_{res}} = 1 // = |H(j\omega)|_{max}$$

(5) (ii) At corner frequencies $|H(j\omega)| \Big|_{\omega=\omega_c} = \frac{|H(j\omega)|_{max}}{\sqrt{2}} = \frac{1}{\sqrt{2}}$

$$\therefore |H(j\omega)| \Big|_{\omega=\omega_c} = \frac{1000\omega_c}{\omega_c^2 + 500^2} = \frac{1}{\sqrt{2}} \quad \omega_c^2 - 1000\sqrt{2}\omega_c + 500^2 = 0 //$$

$$\omega_c = \frac{1000\sqrt{2} \pm \sqrt{(2000)^2 - 4 \times 500^2}}{2} = \frac{1000\sqrt{2} \pm 1000}{2} = 500\sqrt{2} \pm 500 \frac{\text{rad}}{\text{sec}}$$

(10) (i) $|H(\omega)|_{dB} = 20 \log \frac{1000\omega}{\omega^2/500^2}$


$|H(\omega)|_{dB} = 20 \log 1000 + 20 \log \omega - 20 \log (\omega^2/500^2)$ (1)

if $0 < \omega < 500$ $|H(\omega)|_{dB} \approx 20 \log 1000 + 20 \log \omega - 20 \log 500^2$
 $= 20 \log \frac{1000}{500^2} + 20 \log \omega$ (2)

when $\omega = 500$ $|H(\omega)|_{dB} \approx 20 \log 2$ (1)

if $500 \leq \omega$ $|H(\omega)|_{dB} \approx 20 \log 1000 + 20 \log \omega - 40 \log \omega$
 $= 20 \log 1000 - 20 \log \omega$ (2)

when $\omega = 500$ $|H(\omega)|_{dB} \approx 20 \log 2$ (1)

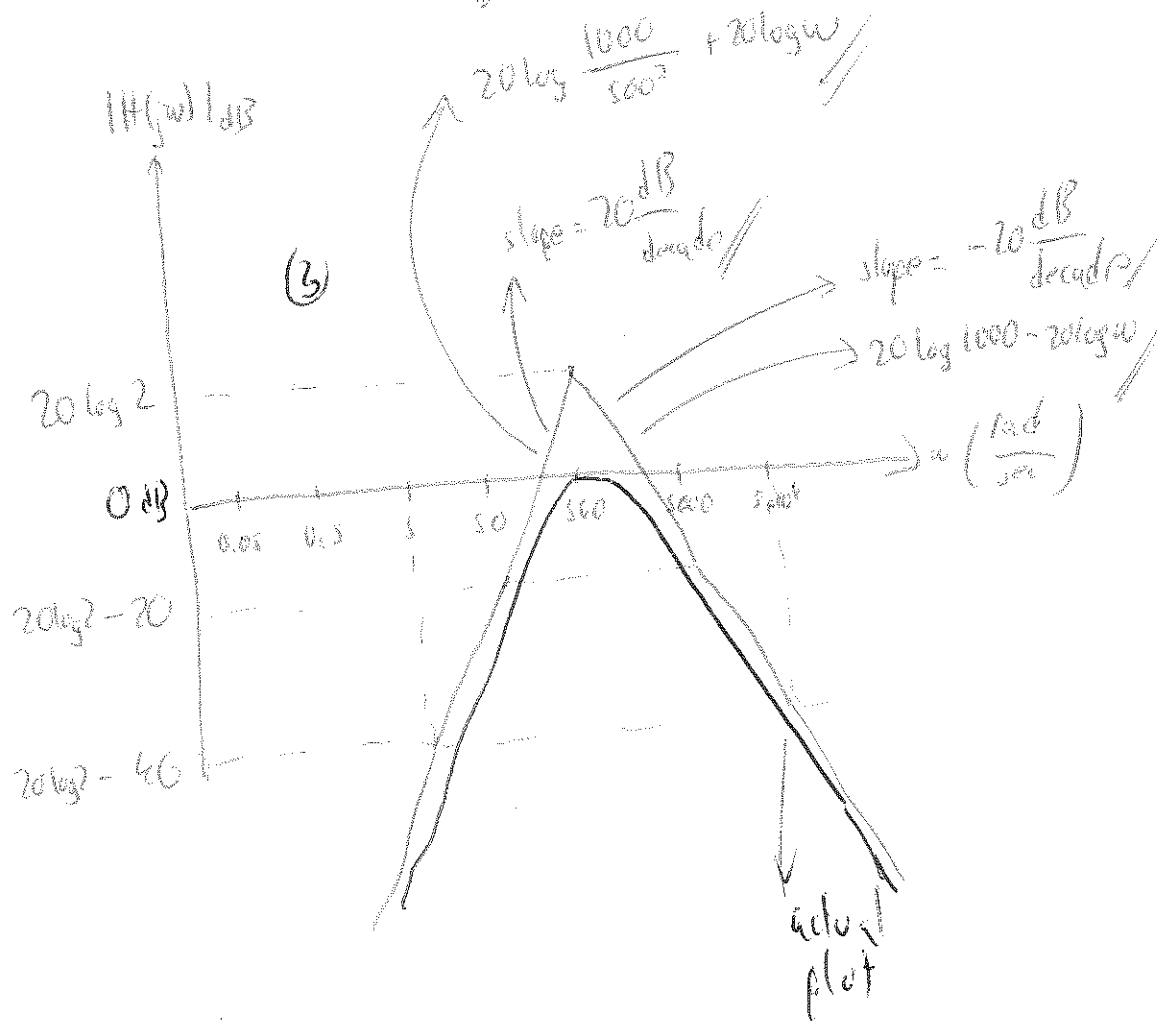

(j) $\angle H(j\omega) = 90 - 2 T_{un}^{-1} \frac{\omega}{500}$

(14) (3) $0 < \omega < \frac{500}{10} \Rightarrow \angle H(j\omega) = 90^\circ$
 (3) $\frac{500}{10} < \omega < 10 + 500 \Rightarrow \angle H(j\omega) = \left[90 - 90 \log \frac{\omega}{50} \right]^\circ$ (linear interpolation in logarithmic scale)

(3) $10 + 500 < \omega \Rightarrow \angle H(j\omega) = 90 - 2 + 90 = -90^\circ$

