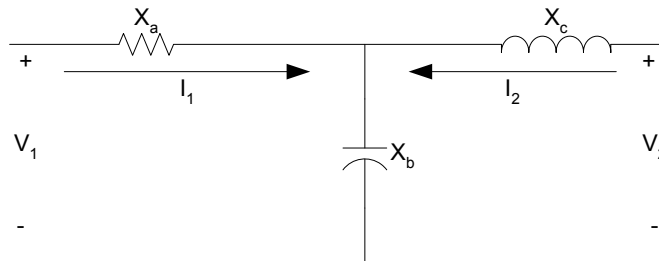


ECE 232 Final

Q1) For the circuit below the impedances of the circuit elements are $X_a=1 \text{ Ohm}$, $X_b=-j \text{ Ohm}$ and $X_c=j \text{ Ohm}$.




The **impedance port equation** for the circuit is given by the formula,

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} r_{11} & r_{12} \\ r_{21} & r_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Find the port parameters r_{11} , r_{12} , r_{21} , r_{22} . **(20 points)**

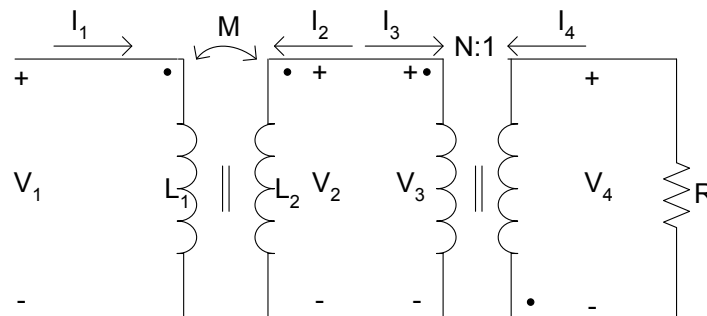Q2) The **time-domain** configuration of a circuit is given as in the figure below.




In **Laplace-domain** the corresponding equations for the coupled inductor and the transformer in this circuit can be written as

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} sL_1 & sM \\ sM & sL_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}, \quad V_3 = -NV_4 \quad \text{and} \quad I_4 = NI_3$$

Find the expression for the input impedance $Z_{in} = \frac{V_1}{I_1}$ of this circuit in **Laplace-domain**. **(20 points)**

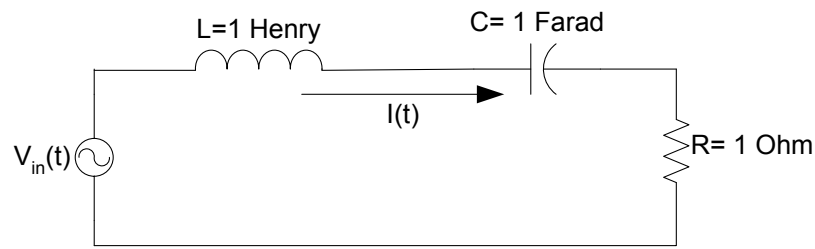
Q3) The **time-domain** configuration of a circuit is given as in the figure below.



The applied input voltage to the circuit is $V_{in}(t) = \sin(\omega t)$ Volt where the angular frequency of the input is $\omega = 1$ rad/sec.

- Find the **sinusoidal steady-state** value of $I(t)$. (15 points)
- What is the average power dissipated over the resistor R ? (5 points)

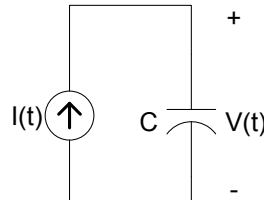
Q4) For the circuit below a capacitor is fed by a current source $I(t)$. Due to this current source the capacitor is charged and its voltage is $V(t)$. Hence $I(t)$ is the input for this circuit and $V(t)$ is the output. The capacitance of the circuit is $C = 1$ Farad.



- Find the transfer function $H(s)$ of this circuit. (3 points)
- Find the impulse response $h(t)$ of this circuit. (3 points)
- Use convolution integral to find $V(t) = \int_{-\infty}^t I(t - \tau)h(\tau)d\tau$ where $I(t) = u(t)$ (unit step function). (14 points)

Q5) For the **balanced three-phase** circuit below, the **source side is delta** connected and the **load side is Y** connected. The source delivers **900 VA complex power** with a **lagging power factor** of $\frac{1}{\sqrt{2}}$. The magnitude of the **source side line-to-line voltage** is $|V_{AB}| = 100\sqrt{3}$

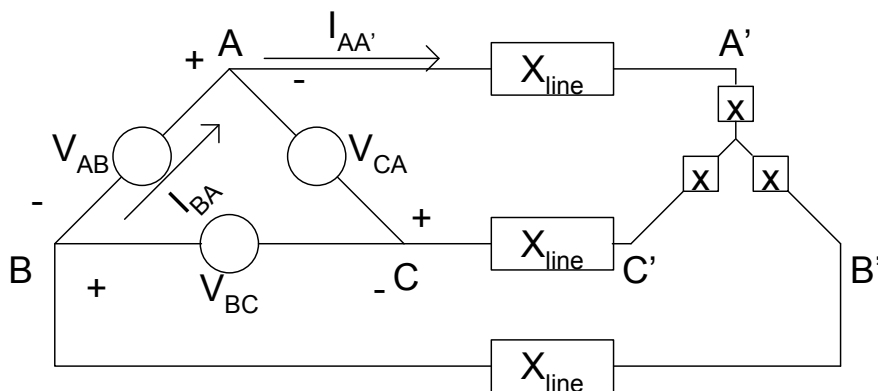Volt (rms). The line impedance is $X_{line} = \frac{50\sqrt{2} - j10\sqrt{2}}{3}$ Ohm.



- Find $|I_{BA}|$, $|I_{AA'}|$, $|V_{A'B'}|$. (16 points)
- Find the load impedance value x . (3 points)
- Is x inductive or capacitive? (1 point)