

Q1

$$V_1 = nV_2$$

$$I_2 = -nI_1$$

$$X_C = \frac{1}{s}$$

$$X_L = s$$

$$n = 0.2$$

$$V_2 = \left[\frac{1}{s} + s \right] (-I_2)$$


$$V_2 = \left[\frac{1+s^2}{s} \right] nI_1$$

$$\frac{V_1}{n} = \frac{1+s^2}{s} nI_1 \Rightarrow \frac{V_1}{I_1} = \left[\frac{1+s^2}{s} \right] n^2$$

$$\frac{V_1}{I_1} = 0.04 \left[\frac{1+s^2}{s} \right]$$

Q2

In Laplace domain
 $X_C = 2s \Omega$

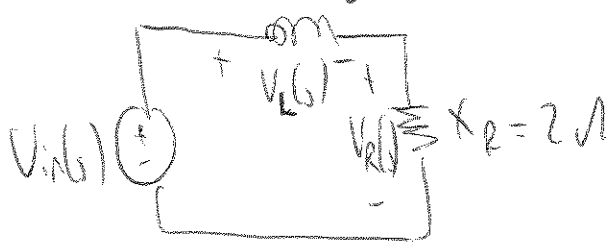



(a) $H(s) = \frac{V_R(s)}{V_{in}(s)} = \frac{2}{2s+2} = \frac{1}{s+1}$

(b) $H(s) = \frac{1}{s+1} \Rightarrow h(t) = \mathcal{L}^{-1} \left\{ \frac{1}{s+1} \right\} = e^{-t} u(t)$


(c) $V_R(t) = \int_{-\infty}^t v_{in}(t-\tau) h(\tau) d\tau = \int_{-\infty}^t h(t-\tau) v_{in}(\tau) d\tau$

$h(t-\tau) = e^{-(t-\tau)} u(t-\tau)$

$v_{in}(\tau) = u(\tau) - u(\tau-1)$

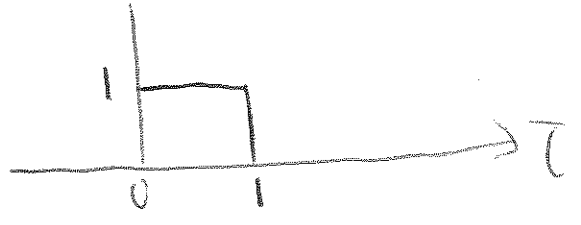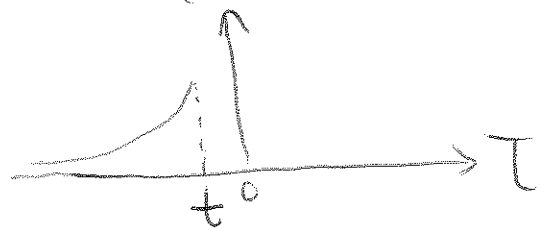


CASE I if $t < 0$

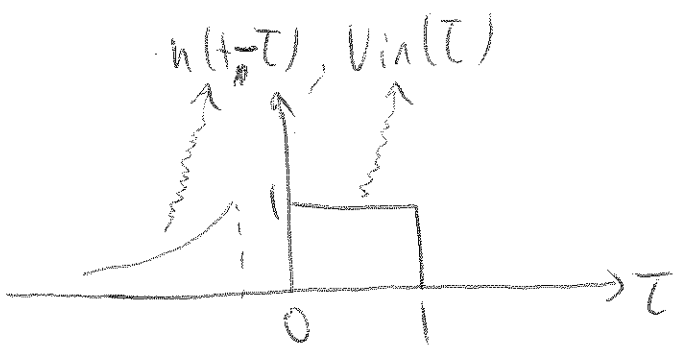


$$V_R(t) = \int_{-\infty}^t h(t-\tau) V_{in}(\tau) d\tau = 0 //$$

Case II $0 \leq t < 1$

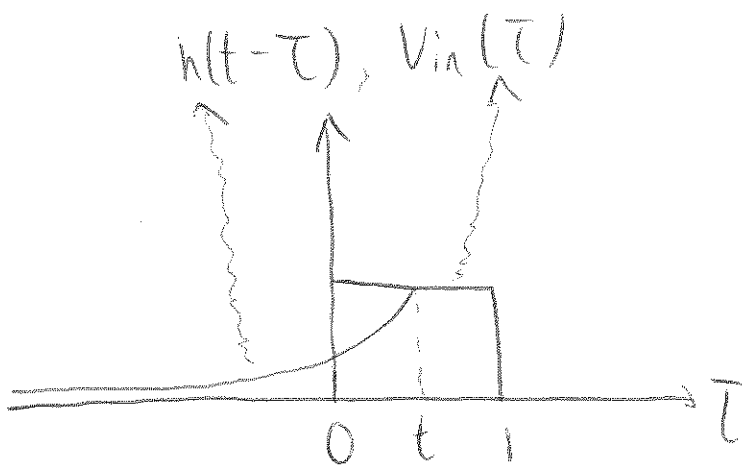


$$\begin{aligned} V_R(t) &= \int_{-\infty}^t h(t-\tau) V_{in}(\tau) d\tau \\ &= \int_0^t e^{-(t-\tau)} u(t-1) d\tau \\ &= \int_0^t e^{-t} e^{\tau} d\tau \\ &= e^{-t} \int_0^t e^{\tau} d\tau \\ &= e^{-t} \left[\frac{e^{\tau}}{1} \right]_0^t = e^{-t} [e^t - 1] \\ &= 1 - e^{-t} // \end{aligned}$$

Case II

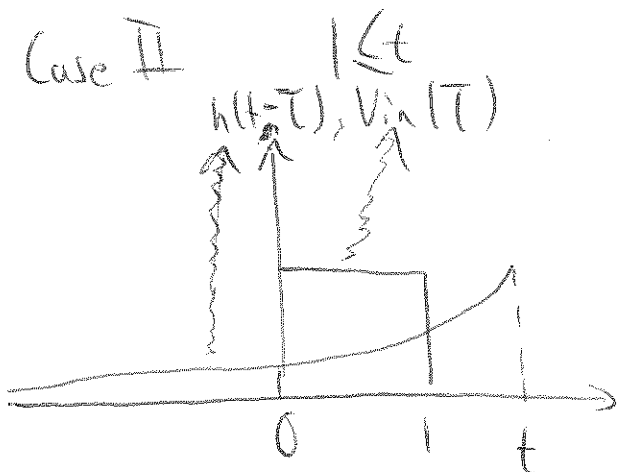

$$\begin{aligned} V_R(t) &= \int_{-\infty}^t h(t-\tau) V_{in}(\tau) d\tau \\ &= \int_0^1 e^{-(t-\tau)} d\tau \\ &= e^{-t} \int_0^1 e^{\tau} d\tau = e^{-t} \left[\frac{e^{\tau}}{1} \right]_0^1 \\ V_R(t) &= e^{-t} [e - 1] // \end{aligned}$$

Q3 In phasor domain

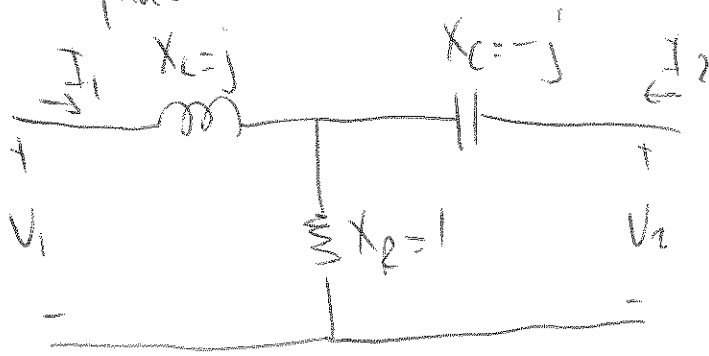

$$V_1 = j I_1 + 1 (I_1 + I_2)$$

$$V_2 = (-j) I_2 + 1 (I_1 + I_2)$$

$$V_1 = [j+1] I_1 + I_2$$

$$V_2 = I_1 + [1-j] I_2$$

$$\Rightarrow Z_{11} = j+1$$

$$Z_{12} = 1$$

$$Z_{21} = 1$$

$$Z_{22} = 1-j$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_1 = X_L I_1 + X_R [I_1 + I_2]$$

$$V_2 = X_C I_2 + X_R [I_1 + I_2]$$

$$\textcircled{Q4} \quad |S_T| = \sqrt{P_T^2 + Q_T^2} = 100\sqrt{2} \text{ VA} //$$

$$|S_T| = 3 |V_{in}| |I_{in}|$$

$$100\sqrt{2} = 3 \times 100 \times |I_{in}| \quad \Rightarrow |I_{in}| = \frac{\sqrt{2}}{3} \text{ Ampere (rms)} //$$

$$P_{\text{loss-line}} = 3 |I_{in}|^2 R_{\text{line}} = 3 \frac{2}{9} \text{ S} = \frac{10}{3} \text{ Watt}$$

$$Q_{\text{loss-line}} = 3 |I_{in}|^2 X_{\text{line}} = 3 \frac{2}{9} \text{ S} = \frac{10}{3} \text{ VAR}$$

$$P_{\text{Load}} = P_T - P_{\text{loss-line}} = 100 - \frac{10}{3} = \frac{290}{3} \text{ Watt}$$

$$Q_{\text{Load}} = Q_T - Q_{\text{loss-line}} = 100 - \frac{10}{3} = \frac{290}{3} \text{ VAR}$$

$$|S_{\text{Load}}| = \sqrt{P_{\text{Load}}^2 + Q_{\text{Load}}^2} = \frac{290}{3} \sqrt{2} \text{ VA}$$

$$|S_{\text{Load}}| = \sqrt{3} |V_{out}| |I_{in}| ~~100\sqrt{2}~~$$

$$\frac{290\sqrt{2}}{3} = \sqrt{3} \frac{\sqrt{2}}{3} V_{out} \quad V_{out} = \frac{290}{\sqrt{3}} \text{ Volt (rms)} //$$

$$|I_{out}| = \frac{|I_{in}|}{\sqrt{3}} = \frac{\sqrt{2}}{3\sqrt{3}} \text{ Ampere (rms)} //$$

$$Z_e \{X_{\text{Load}}\} = \frac{P_{\text{Load}}}{3 |I_{out}|^2} = \frac{\frac{290\sqrt{2}}{3}}{3 \frac{2}{27}} \Omega, \quad I_m \{X_{\text{Load}}\} = \frac{Q_{\text{Load}}}{3 |I_{out}|^2} = \frac{\frac{290\sqrt{2}}{3}}{3 \frac{2}{27}}$$

$$X_{\text{Load}} = \frac{870}{\sqrt{2}} + j \frac{870}{\sqrt{2}} \Omega //$$