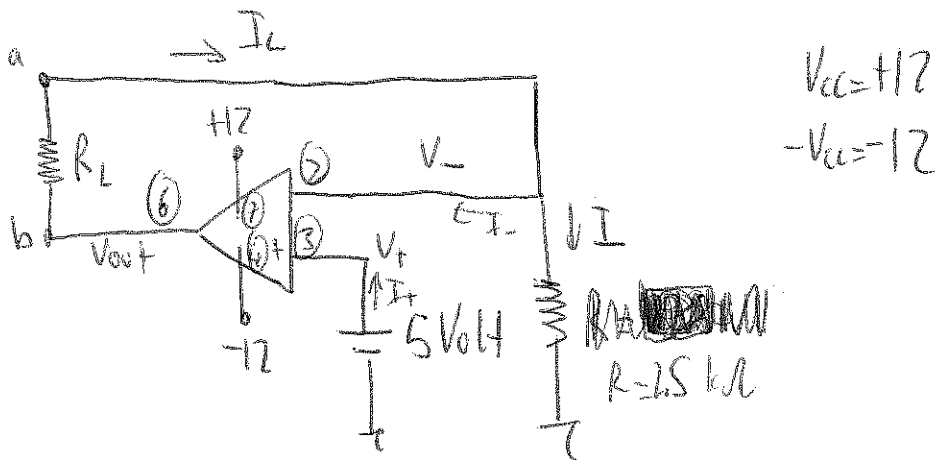


### 3- Miscellaneous OP-AMP circuits

#### ① Constant current source



The opamp has two operation regions

\* In linear region  $V_- = V_+ = 5 \text{ Volt}$

\* In positive saturation region  $V_{out}$  becomes  $V_{out} = V_{cc} = +12 \text{ Volt}$

— In linear region

$$V_+ = V_- = 5 \text{ Volt} \quad I_+ = I_- \approx 0 \quad \text{and} \quad I_L = I = \frac{V_-}{R} = \frac{5}{R}$$

\* In linear region the current ~~that~~ changes and it is  $I = \frac{5}{R}$

— In (+) saturation region  $V_+ \geq V_{sat} = 12 \text{ Volt}$ , and  $I_- \neq 0$

$$I_L = I + I_-$$

in order to find the limit value  $R_{max}$  we take  $I_- \approx 0$  Amperes

$$\text{hence } I_L \approx I \quad \frac{V_{out} - V_-}{R_{Lmax}} = \frac{V_-}{R} \quad V_- = \frac{V_{out} R}{R + R_{Lmax}}$$

when  $I_- = 0$  Ampere  $V_{out} = 12 \text{ Volt}$ ;  $V_- = 5 \text{ Volt}$

$$V_+ \geq V_- = \frac{V_{out} R}{R + R_{max}}$$

$$\Rightarrow \frac{12 \times 2.5}{2.5 + R_{max}}$$

$$5 R_{max} \geq 30 - 12.5$$

$$5 R_{max} \geq 17.5$$

$$R_{max} \geq 3.5 \text{ k}\Omega$$

### Result

\* if  $0 < R_L < R_{max}$ , the circuit is in linear region

$$I_+ \approx I_- \approx 0 \quad I = \frac{V_-}{2.5 \text{ k}\Omega}, \quad V_+ = V_- = 5, \quad I = \frac{5}{2.5 \text{ k}\Omega} = 2 \text{ mA (constant current source)}$$


,  $V_{out} < V_{cc}$ ,  
12 Volt

\* if  $R_L > R_{max}$ , the circuit is in positive saturation region

$$I_- \approx 0 \quad I = I_L + I_- \quad V_+ > V_- \quad I = \frac{V_-}{R} = \frac{V_{cc}}{R_L + R} \quad \left( \text{NO MORE CONSTANT CURRENT} \right)$$

$5 > V_-$

## 2 - Sinusoidal Oscillator

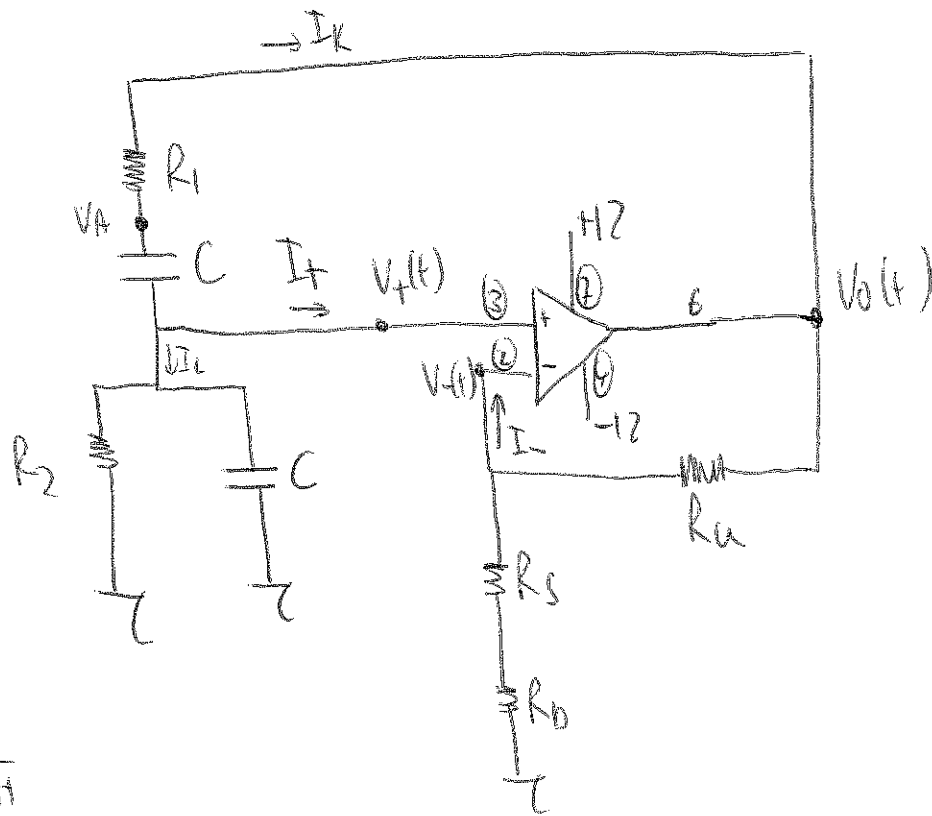

$$I_+ \approx I_- \approx 0 \text{ Ampere}$$

$$V_+ = V_-$$

(in linear region)

Hence

$$V_- = V_+ = V_0 \frac{R_2 + R_b}{R_1 + R_2 + R_b}$$

$$D = \frac{d}{dt}$$

$$I_K + I_L + I_+ = 0 \quad \xrightarrow{I_+ \approx 0} \quad I_K + I_L = 0$$

$$I_L = \frac{V_+}{R_2} + C \frac{dV_+}{dt}$$

$$I_K = C \frac{d(V_+ - V_A)}{dt} = \frac{V_A - V_0}{R_1}$$

$$I_L = \left[ \frac{1}{R_2} + CD \right] V_+$$

$$C \frac{dV_+}{dt} - C \frac{dV_A}{dt} = \frac{V_A}{R_1} - \frac{V_0}{R_1}$$

$$C \frac{dV_+}{dt} + \frac{V_0}{R_1} = C \frac{dV_A}{dt} + \frac{V_A}{R_1}$$

$$CDV_+ + \frac{1}{R_1} V_0 = \left( CD + \frac{1}{R_1} \right) V_A$$

$$I_L = \left[ \frac{1}{R_2} + CD \right] \frac{R_1 R_b}{R_1 + R_2 + R_b} V_0$$

$$V_A = \frac{CDV_+ + \frac{1}{R_1}V_0}{CD + \frac{1}{R_1}} \Rightarrow I_L = \frac{V_A - V_0}{R_1}$$

$$V_A = \frac{R_1CDV_+ + V_0}{R_1CD + 1} \quad I_L = \frac{\frac{R_1CDV_+ + V_0}{R_1CD + 1} - V_0}{R_1}$$

$$V_0 - V_+ = V_0 \frac{R_a}{R_a + R_s + R_b}$$

$$I_L = \frac{R_1CDV_+ - R_1CDV_0}{R_1[R_1CD + 1]}$$

$$I_L = -I_K$$

$$\left[ \frac{1}{R_2} + CD \right] \frac{R_s + R_b}{R_a + R_s + R_b} V_0 = \frac{R_1CD [V_0 - V_+]}{R_1 [R_1CD + 1]}$$

$$\left[ \frac{1 + R_2CD}{R_2} \right] \frac{R_s + R_b}{R_a + R_s + R_b} V_0 = \frac{C R_a D V_0}{R_1 [R_1CD + 1]}$$

$$[1 + R_2CD](R_s + R_b)[R_1CD + 1]V_0 = R_a R_2 C D V_0$$

$$(R_s + R_b)R_1R_2C^2(D^2V_0) + \left[ (R_s + R_b)(R_1C + R_2C) - R_aR_2C \right] DV_0 + (R_s + R_b)V_0 = 0$$

$$R_1R_2C^2 \frac{d^2V_0}{dt^2} + \left[ (R_1 + R_2) - \frac{R_aR_2}{R_s + R_b} \right] C \frac{dV_0}{dt} + V_0 = 0$$

$$* \frac{d^2 V_0}{dt^2} + \frac{C \left[ (R_1 + R_2) - \frac{R_a R_z}{R_s + R_b} \right]}{R_1 R_2 C^2} \frac{dV_0}{dt} + \frac{1}{R_1 R_2 C^2} V_0 = 0$$

if  $R_1 + R_2 = \frac{R_a R_z}{R_s + R_b}$  then \* turns to


$$\frac{d^2 V_0}{dt^2} + \frac{1}{R_1 R_2 C^2} V_0 = 0 \quad **$$

The solution of \*\*

$$V_0(t) = K_1 \sin(\omega t) + K_2 \cos(\omega t) \quad \left[ \begin{array}{l} \text{A sinusoidal} \\ \text{oscillator} \end{array} \right]$$

$$\omega = \sqrt{\frac{1}{R_1 R_2 C^2}} = \frac{1}{C \sqrt{R_1 R_2}}$$

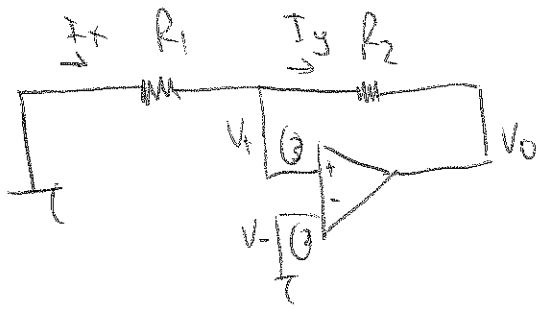③ Creating Hysteresis Loop using bistable circuit



$I_x = I_y$  in linear region


$$\frac{0 - V_+}{R_1} = \frac{V_+ - V_0}{R_2}$$

$$V_+(R_1 + R_2) = V_0 R_1$$

$$V_+ = \frac{R_1}{R_1 + R_2} V_0$$

$$V_+ = \beta V_0 \quad \beta = \text{feed-fraction}$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

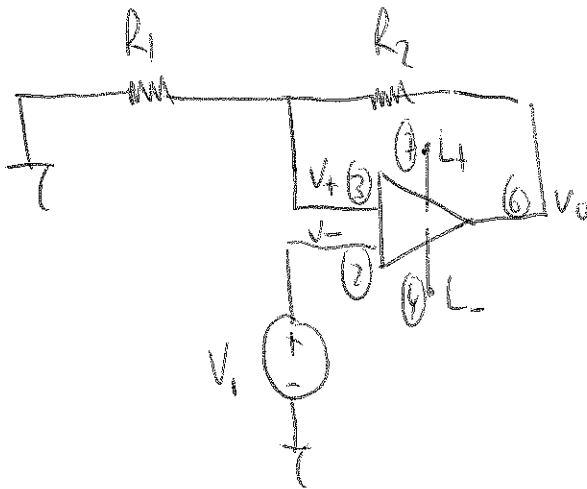

$$L_+ = 12 \text{ Volt}$$

$$L_- = -12 \text{ Volt}$$


if  $V_0 = L_+ \Rightarrow V_+ = \beta L_+$  now increase  $V_I$  if  $V_I$  exceeds  $V_+ = \beta L_+$  then  $V_- > V_+$  and  $V_0 = L_-$ ; if  $V_0 = L_-$

then  $V_+ = \beta L_-$

if  $V_0 = L_- \Rightarrow V_+ = \beta L_-$  now decrease  $V_I$  if  $V_I$  becomes lower than  $V_+ = \beta L_-$  then  $V_- < V_+$  and  $V_0 = L_+$ ; if  $V_0 = L_+$

then  $V_+ = \beta L_+$

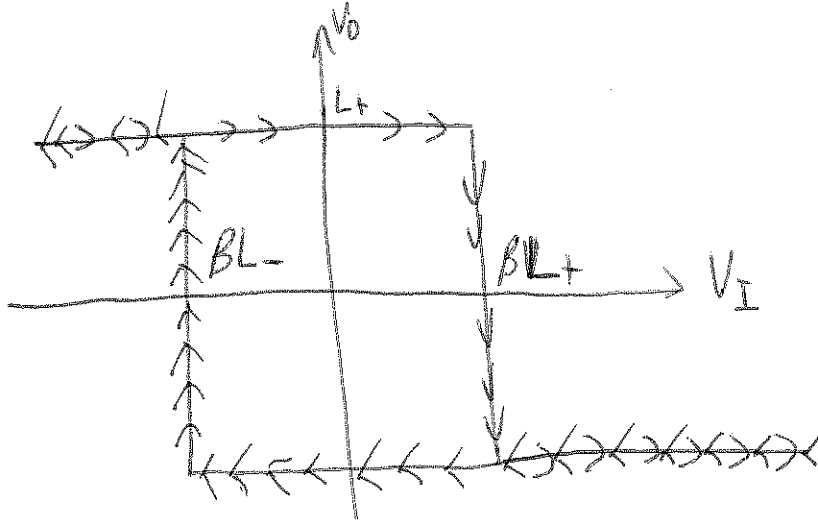the characteristics of  
bistable circuit




$$\beta = \frac{R_1}{R_1 + R_2}$$

$$L_+ = 12 \text{ Volt}$$

$$L_- = -12 \text{ Volt}$$

4- Inductor using two opamps

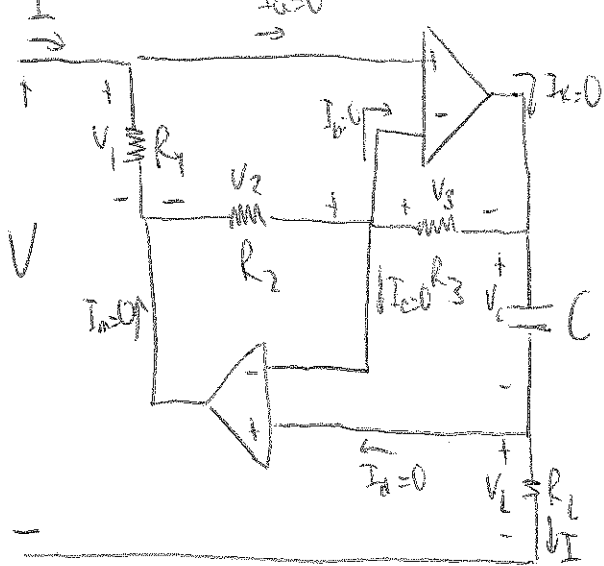

$$V_1 = V_2$$

$$V_3 + V_c = 0$$

$$V_c = R_L I \quad I = C \frac{dV_c}{dt}$$

~~$$V_c = R_L C \frac{dV_c}{dt}$$~~

$$V_c = R_L C \frac{dV_c}{dt} \rightarrow V_c = -V_c$$

$$V_c = -R_L C \frac{dV_3}{dt} \quad V_3 = I R_3$$

$$V_c = -R_L C R_3 \frac{dI}{dt} \quad V_2 = -I R_2 \quad V_c = -\frac{R_L C R_3}{R_2} \left( \frac{d(-I R_2)}{dt} \right)$$

$$V_c = \frac{R_L C R_3}{R_2} \frac{dI}{dt}$$

$$V_c = \frac{R_L C R_3}{R_2} \frac{dV_1}{dt}$$

$$V_c = \frac{R_L C R_3 R_1}{R_2} \frac{dI}{dt}$$

$$V_1 = R_1 I$$

$$V_c = V = \frac{R_L C R_3 R_1}{R_2} \frac{dI}{dt}$$

$$L = \frac{R_L C R_3 R_1}{R_2}$$