

(Q1)

In ~~Time~~ Domain

ECE 232 Midterm  
2014-2015

Page 1

$$V_{in} = V_R + V_L + V_C$$

$$C \frac{dV_C}{dt} = I_L \xrightarrow{\mathcal{L}} C[sV_C(s) - V_C(0)] = I_L(s)$$

$$V_{in} = RI_L + L \frac{dI_L}{dt} + V_C$$

$$I_L(s) = 0.2[sV_C(s) - V_C(0)]$$

if

$$V_{in}(s) = RI_L(s) + L[sI_L(s) - I_L(0)] + V_C(s)$$

diff denominator 5

$$V_{in}(s) = 6I_L(s) + [sI_L(s) - I_L(0)] + V_C(s)$$

$$V_{in}(s) = [6 + s]I_L(s) - I_L(0) + V_C(s)$$

$$V_{in}(s) = [6 + s]0.2[sV_C(s) - V_C(0)] - I_L(0) + V_C(s)$$

$$V_{in}(s) = [0.2s^2 + 1.2s + 1]V_C(s) - 0.2[6 + s]V_C(0) - I_L(0)$$

$$V_C(s) = \frac{0.2(6 + s)V_C(0) + I_L(0)}{0.2s^2 + 1.2s + 1} + \frac{V_{in}(s)}{0.2s^2 + 1.2s + 1}$$

laplace denominator s

$$V_C(s) = \frac{(6 + s)V_C(0) + sI_L(0)}{s^2 + 6s + 5} + \frac{s V_{in}(s)}{s^2 + 6s + 5}$$

~~Answer~~

(a) If  $I_L(0) = 0$  Ampere and  $V_C(0) = 0$  Volt

$$V_C(s) = \frac{s}{s^2 + 6s + 5} V_{in}(s) \quad \text{if } V_{in}(t) = u(t) \xrightarrow{\mathcal{L}} V_{in}(s) = \frac{1}{s}$$

$$V_C(s) = \frac{s}{s^2 + 6s + 5} \cdot \frac{1}{s} = \frac{1}{s^2 + 6s + 5} = \frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+5} \quad (2) \text{ part}$$

$$s = A(s+1)(s+5) + B(s)(s+5) + C(s)(s+1)$$

$$s = (A+B+C)s^2 + (6A+5B+C)s + 5A$$

$$A = 1$$

6 part

$$B = \frac{5}{4}$$

$$C = \frac{1}{4}$$

$$\begin{aligned} A+B+C=0 &\longrightarrow B+C+1=0 & B+C &= -1 \\ 6A+5B+C=0 &\longrightarrow 6+5B+C=0 & 5B+C &= -6 \end{aligned}$$

A=1 B=-5/4 C=1/4

Vc(s) = 1/s - 5/4 \* 1/(s+1) + 1/4 \* 1/(s+5) -> Vc(t) = u(t) - 5/4 e^-t u(t) + 1/4 e^-5t u(t) = [1 - 5/4 e^-t + 1/4 e^-5t] u(t) 2 part

(b) If Vx(t)=0, Vc(0)=2 Volt, Ic(0)=0 Ampere

Vc(s) = (2(s+6)+0) / (s^2+6s+5) = 2s+12 / (s^2+6s+5) = A/(s+1) + B/(s+5)

2s+12 = A(s+5) + B(s+1)

2s+12 = (A+B)s + (A+5B)

A+B=2

A+5B=12

B=5/2

A=-1/2


Vc(s) = -1/2 \* 1/(s+1) + 5/2 \* 1/(s+5) = [-1/2 e^-st + 5/2 e^-5t] u(t) 3 part

Q2

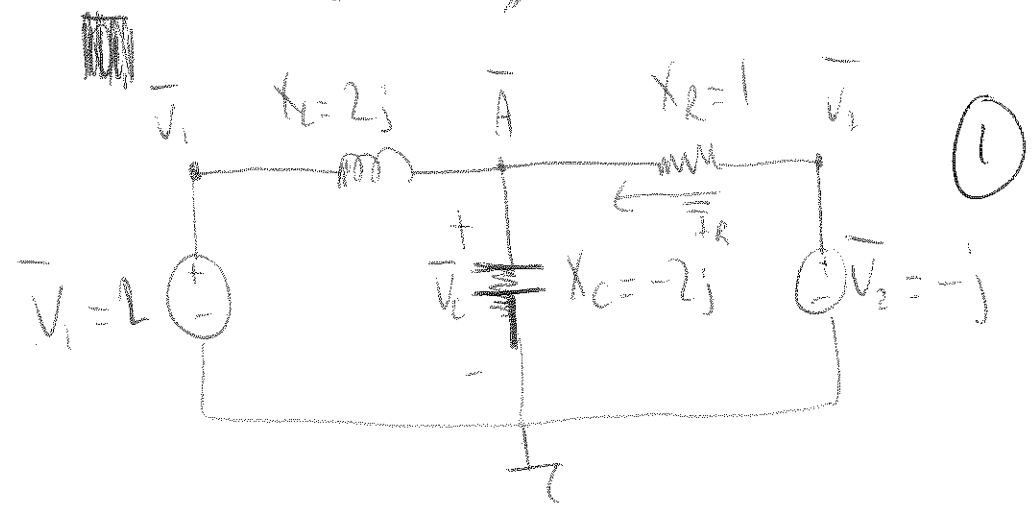a)  $V_1(t) = 2 \cos(t)$   $V_2(t) = \sin(t)$   
 $\downarrow$   $\omega_1 = 1 \frac{\text{rad}}{\text{sec}}$   $\downarrow$   $\omega_2 = 1 \frac{\text{rad}}{\text{sec}}$   $\omega = \omega_1 = \omega_2 = 1 \frac{\text{rad}}{\text{sec}}$  (same)

Use phasors

$\bar{V}_1 = 2$ ,  $\bar{V}_2 = -j$ ,  $X_R = 1$ ,  $X_C = j\omega L = j\omega = 2j$   
 $X_C = \frac{1}{j\omega C} = \frac{1}{j\omega C} = \frac{1}{j \times 1 \times 0.5} = -2j$  (3)



$\frac{\bar{V}_1 - \bar{A}}{2j} + \frac{\bar{V}_2 - \bar{A}}{1} = \frac{\bar{A}}{X_C}$   $\frac{2 - \bar{A}}{2j} + \frac{-j - \bar{A}}{1} = \frac{\bar{A}}{-2j}$  (3)


$2 - \bar{A} + 2 - 2j\bar{A} = -\bar{A}$   $4 = 2j\bar{A}$   $\bar{A} = \frac{2}{j} = -2j$

(1)  $\bar{V}_C = \bar{A} = -2j \Rightarrow V_C(t) = -2 \cos(t + 90^\circ)$  Volt (At sinusoidal steady-state)

$\bar{I}_R = \frac{\bar{V}_2 - \bar{A}}{X_R} = \frac{-j - (-2j)}{1} = \frac{j}{1} = j$   $P_R = \frac{1}{2} R \bar{I}_R \bar{I}_R^* = \frac{1}{2} \times 1 (j)(j)$   
 $= \frac{1}{2} \times j^2 = \frac{1}{2} \text{ Watt}$  (1)

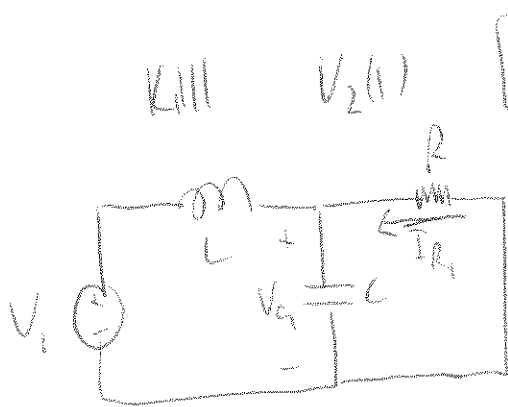(b)  $V_1(t) = \cos(t)$   
 $\downarrow$   
 $\omega_1 = 1 \frac{\text{rad}}{\text{sec}}$

$V_2(t) = \sin(2t)$   
 $\downarrow$   
 $\omega_2 = 2 \frac{\text{rad}}{\text{sec}}$       $\omega_1 \neq \omega_2$



Phasor


$X_L = j\omega_1 L = 2j \Omega$

$X_C = \frac{1}{j\omega_1 C} = \frac{1}{j} = -2j \Omega$

3 pm

$X_R = 1 \Omega$

$\bar{V}_1 = 1$

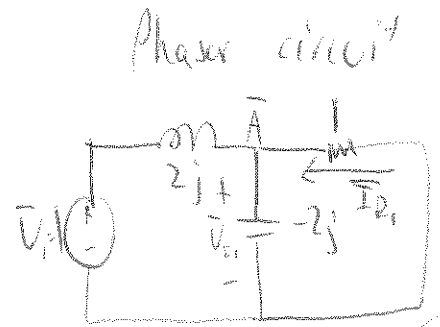

2 pm

$\frac{\bar{V}_1 - \bar{A}}{2j} = \frac{\bar{A}}{-2j} + \frac{\bar{A}}{1}$

$\bar{V}_1 - \bar{A} = -A + \bar{A} 2j \rightarrow 1 = 2j \bar{A}$

$\bar{A} = \frac{1}{2j} = \frac{-j}{2} = -\frac{j}{2} = \bar{V}_C$  (1 pm)

$V_C(t) = -\frac{1}{2} \cos(t + 90^\circ)$  Volt

1 pm


$\bar{I}_{R_1} = \frac{0 - \bar{A}}{1} = \frac{0 - (-\frac{j}{2})}{1} = \frac{j}{2}$

$P_{R_1} = \frac{1}{2} R \bar{I}_{R_1} \bar{I}_{R_1}^* = \frac{1}{2} \times 1 \times \left(\frac{j}{2}\right) \left(-\frac{j}{2}\right)$

$= \frac{1}{8} \text{ Watt}$

1 pm

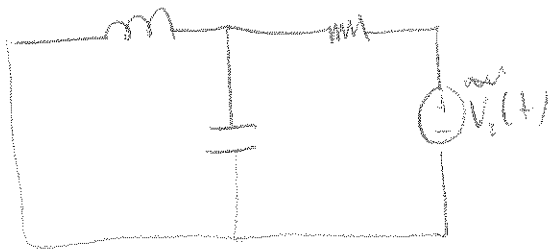Kill  $V_1(t)$   $[V_2(t) = \sin(2t)]$   
 $\omega = 2 \frac{\text{rad}}{\text{s}}$




Phasor  
 $\vec{V}_2 = -j \text{ Volt}$

$R = 1 \Omega$

$X_C = \frac{1}{j\omega C} = \frac{1}{j \cdot 2 \cdot 0.5} = -j$

$X_L = j\omega L = 4j$

Phasor circuit

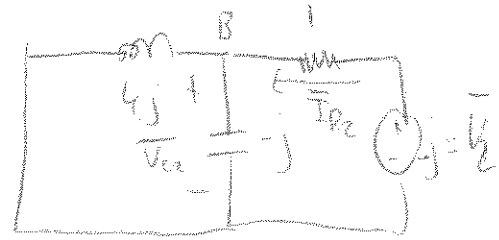

3 puca

3 puca

$$\frac{\vec{V}_2 - \vec{B}}{1} = \frac{\vec{B}}{j} + \frac{\vec{B}}{4j}$$

(4j)      (-4)

$$(-j - \vec{B}) 4j = -4\vec{B} + \vec{B}$$

$$4 = [4j - 3] \vec{B}$$

$$\vec{B} = \frac{4}{4j - 3} = \frac{-4}{3 - 4j}$$

$$\vec{B} = \frac{-4(3 + 4j)}{(3 - 4j)(3 + 4j)} = \frac{-4(3 + 4j)}{25} = -\frac{4}{5} \left[ \frac{3 + 4j}{5} \right]$$

$$\vec{V}_{C2} = \vec{B} \Rightarrow V_{C2}(t) = -\frac{4}{5} \cos(2t + \tan^{-1} \frac{4}{3})$$

$$\vec{I}_{R2} = \frac{-j - \vec{B}}{1} = \frac{-j - \left[ -\frac{4}{25}(3 + 4j) \right]}{1} = \frac{-j + \frac{4}{25}(3 + 4j)}{1} = \frac{-25j + 12 + 16j}{25}$$

$$\vec{I}_{R2} = \frac{12 + 9j}{25} = \frac{3}{5} \left[ \frac{4 + 3j}{5} \right]$$

$$P_{R2} = \frac{1}{2} R \vec{I}_{R2} \vec{I}_{R2}^* = \frac{1}{2} \times 1 \times \frac{3}{5} \left[ \frac{4 + 3j}{5} \right] \cdot \frac{3}{5} \left[ \frac{4 - 3j}{5} \right] = \frac{3 \times 3 \times 25}{2 \times 25 \times 25} = \frac{9}{50}$$

9 puca

$$V_c(t) = V_{c_1}(t) + V_{c_2}(t)$$

$$= -\frac{1}{2} \cos(t + 90^\circ) - \frac{4}{5} \cos\left(2t + \tan^{-1} \frac{4}{3}\right)$$

(puan)

$$P_R = P_{R_1} + P_{R_2} = \frac{1}{8} + \frac{9}{50} = \frac{25 + 36}{200} = \frac{61}{200} \text{ Watt}$$

(puan)


Q3)  $H(\omega) = 5 \frac{(\omega + 10)}{(\omega + 50)}$

$H(j\omega) = 5 \frac{(j\omega + 10)}{j\omega + 50}$

(a)  $|H(j\omega)| = 5 \frac{\sqrt{\omega^2 + 10^2}}{\sqrt{\omega^2 + 50^2}}$   
 (3)

(b)  $\angle H(j\omega) = \tan^{-1} \frac{\omega}{10} - \tan^{-1} \frac{\omega}{50}$   
 (3)

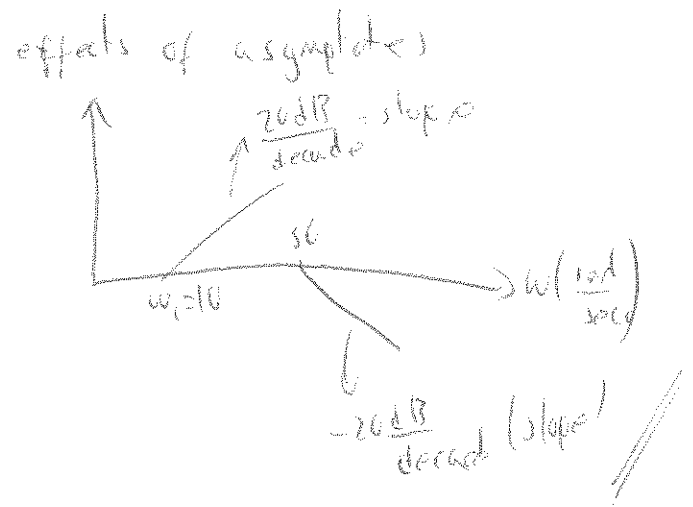(c) zero  $z_1 = -10 \Rightarrow \omega_1 = 10 \frac{\text{rad}}{\text{sec}}$   
 pole  $p_1 = -50 \Rightarrow \omega_2 = 50 \frac{\text{rad}}{\text{sec}}$



if  $0 < \omega < 10 = \omega_1$

$|H(j\omega)| \approx 5 \times \frac{10}{50} = 1 \Rightarrow 20 \log |H(j\omega)| \approx 20 \log 1 = 0 \text{ dB}$   
 (3)

if  $\omega_1 < \omega < \omega_2 \Rightarrow$


$|H(j\omega)| \approx 5 \frac{\omega}{50} = \frac{\omega}{10} \Rightarrow 20 \log |H(j\omega)| = 20 \log \omega - 20 \log 10$   
 (3)

$|H(j\omega)|_{\text{dB}} \approx 20 \log 10 - 20 \log 10 = 0 \text{ dB}$


$|H(j\omega)|_{\text{dB}} \approx 20 \log 50 - 20 \log 10 = 20 \log 5$

if  $\omega < \omega_2 = 50$

$|H(j\omega)| \approx 5 \frac{\omega}{\omega} = 5$        $|H(j\omega)|_{dB} = 20 \log |H(j\omega)| \approx 20 \log 5$  (2)

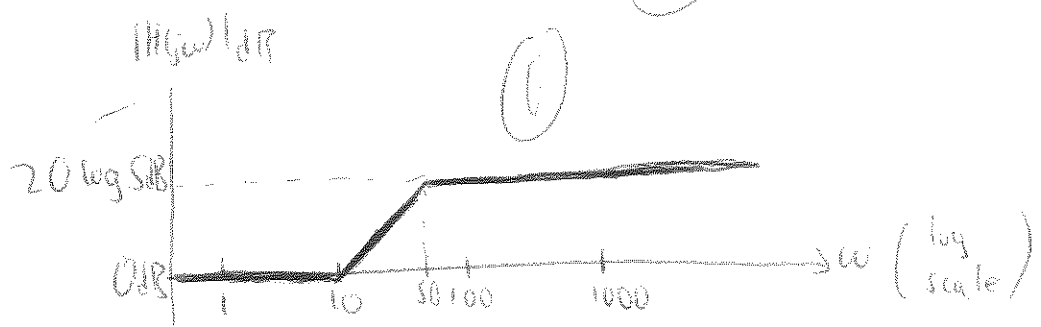

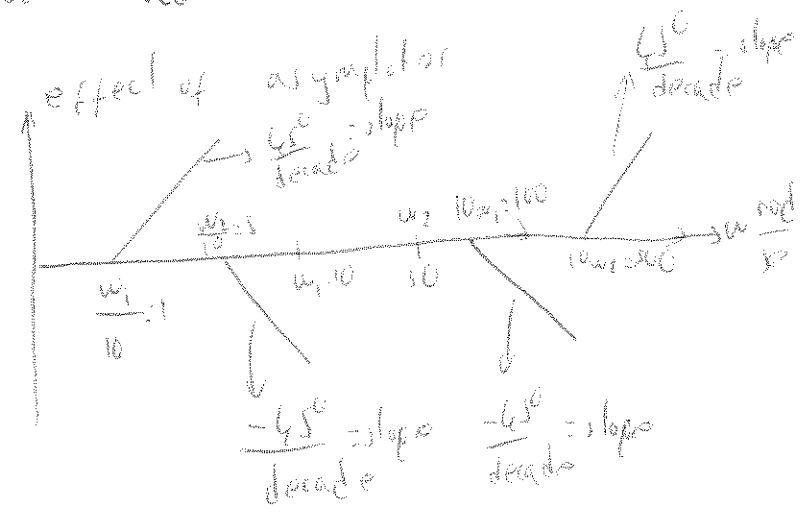(d) zero  $z_1 = 10 \Rightarrow \omega_1 = 10 \frac{\text{rad}}{\text{sec}}$   
 pole  $p_1 = 50 \Rightarrow \omega_2 = 50 \frac{\text{rad}}{\text{sec}}$



$0 < \omega < \frac{\omega}{10} = 1$        $|H(j\omega)| = 0$  (1)

$1 = \frac{\omega_1}{10} < \omega < \frac{\omega_2}{10} = 5$        $|H(j\omega)| \approx 0 + 45 \log \frac{\omega}{\frac{\omega_1}{10}} = 45 \log \frac{\omega}{10} = 45 \log \omega$

$\omega = \frac{\omega_1}{10} = 1$        $|H(j\omega)| = 0$  (2)

$\omega = \frac{\omega_2}{10} = 5$        $|H(j\omega)| = 45 \log 5$

$\frac{\omega_2}{10} < \omega < 10 \omega_1$        $|H(j\omega)| = 45 \log 5$  (1)

$5 < \omega < 100$



$$10w_1 < w < 10w_2$$

$$100 < w < 500$$


$$|H(j\omega)| = 45 \log 5 - 45 \log \frac{\omega}{10w_1} = 45 \log 5 - 45 \log \frac{\omega}{100}$$

$$w = 500 \quad |H(j\omega)| = 45 \log 5 - 45 \log \frac{500}{100} = 0$$

(2)

Page 9

$$500 = 10w_2 < w \Rightarrow |H(j\omega)| = 0$$

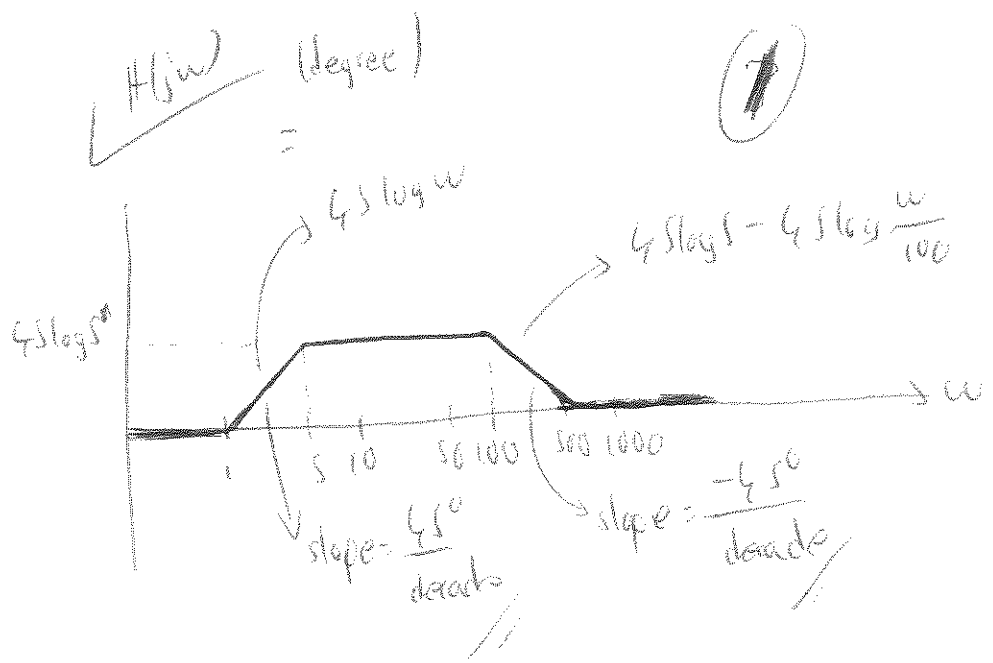

$$(4) H(s) = \frac{s^2 + 1600}{s^2 + 100s + 1600} = \frac{s^2 + 1600}{s^2 + 2D\omega_0 s + \frac{40^2}{\omega_0^2}}$$

$$(a) H(j\omega) = \frac{1600 - \omega^2}{1600 - \omega^2 + 100j\omega}$$

$$|H(j\omega)| = \frac{|1600 - \omega^2|}{\sqrt{[1600 - \omega^2]^2 + [100\omega]^2}} \quad (3)$$

$$(b) 0 < \omega < 40 \Rightarrow |H(j\omega)| = -\text{Tan}^{-1} \frac{100\omega}{1600 - \omega^2} \quad (3)$$

$$40 < \omega \Rightarrow |H(j\omega)| = 180 - \text{Tan}^{-1} \frac{100\omega}{1600 - \omega^2}$$

$$(c) \text{ if } |H(j\omega)| \text{ is minimized } |1600 - \omega^2| = 0 \quad \omega = 40 \frac{\text{rad}}{\text{sec}}$$

$$\text{if } \omega = 40 \frac{\text{rad}}{\text{sec}} \quad |H(j\omega)| = 0 \quad (2)$$

$$(d) 2D\omega_0 = 100 \quad 2D(40) = 100 \quad D = \frac{100}{80} = \frac{5}{4} = 1.25 \quad (2)$$

$$(e) \text{ if } \omega = 0 \quad |H(j\omega)| = 1 = |H(j\omega)|_{\text{max}}$$

$$\text{if } \omega \rightarrow \infty \quad |H(j\omega)| = 1 = |H(j\omega)|_{\text{max}}$$

$$\text{at } \omega_{c1} = \omega_{c2} \quad |H(j\omega)| = \frac{|H(j\omega)|_{\text{max}}}{\sqrt{2}} = \frac{1}{\sqrt{2}}$$

$$\frac{|1600 - \omega_c^2|}{\sqrt{[1600 - \omega_c^2]^2 + [100\omega_c]^2}} = \frac{1}{\sqrt{2}} \quad (2)$$

$$2(1600 - w_c^2)^2 = (1600 - w_c^2)^2 + (100w_c)^2$$

$$(1600 - w_c^2)^2 = (100w_c)^2$$

$$w_c^2 + 100w_c - 1600 = 0$$

$$1600 - w_c^2 = \pm 100w_c$$

$$w_c = \frac{\pm 100 \pm \sqrt{(100)^2 + 4 \cdot 1600}}{2} = \frac{\pm 100 \pm \sqrt{16400}}{2}$$

$$w_{c1} = 50 + 5\sqrt{164}$$

$$w_{c2} = 5\sqrt{164} - 50$$

$$w_{c3} = 50 + 10\sqrt{41}$$

$$(2) w_{c4} = 10\sqrt{41} - 50$$

