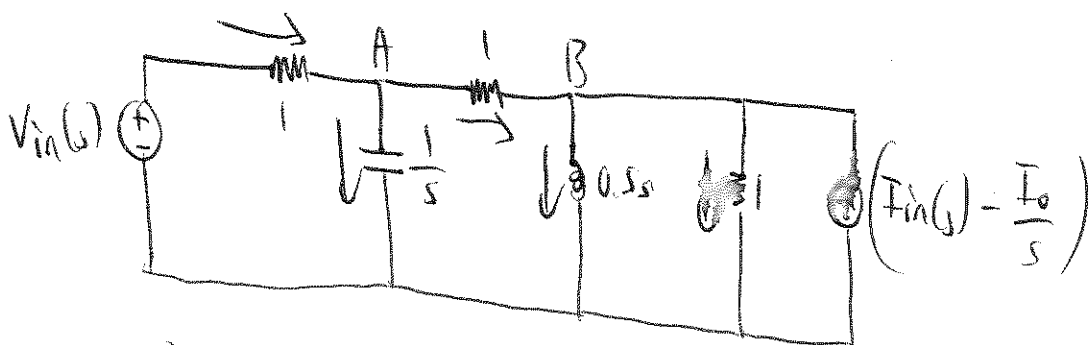


$$L \frac{dI_L}{dt} = V_L \quad L \left[ sI_L(s) - I_0 \right] = V_L(s) \quad \frac{V_L(s)}{L} + I_0 = sI_L(s)$$

$$\textcircled{1} I_L(s) = \frac{V_L(s)}{sL} + \frac{I_0}{s}$$

(b)

Carry the current source  $\frac{I_0}{s}$  near to  $I_{in}(s)$



$$A = V_C(s)$$

(5)

$$\frac{V_{in} - A}{1} = \frac{A}{1} + \frac{A - B}{1/s}$$

(5)

$$\frac{A - B}{1} + I_{in}(s) - \frac{I_0}{s} = \frac{B}{0.5s} + \frac{B}{1}$$

$$V_{in} - A = sA + A - B$$

$$V_{in} = (2 + s)A - B$$

$$I_{in}(s) - \frac{I_0}{s} = \left( 2 + \frac{2}{s} \right) B - A$$

$$I_{in}(s) - \frac{I_0}{s} = \frac{2s + 2}{s} B - A$$

(2)

$$\frac{s I_{in}(s) - I_0}{2s + 2} + \frac{sA}{2s + 2} = B$$

Q-1 - (Continue)

$$V_{in} = (2s)A - \left[ \frac{s}{2s+2} I_{in} - \frac{I_0}{2s+2} + \frac{sA}{2s+2} \right]$$

$$V_{in} + \frac{s}{2(s+1)} I_{in} - \frac{I_0}{2(s+1)} = (2s)A - \frac{sA}{2(s+1)}$$

$$V_{in} + \frac{s}{2(s+1)} I_{in} - \frac{I_0}{2(s+1)} = \frac{2(s^2 + 3s + 2) - s}{2(s+1)} A$$

$$V_{in} + \frac{s}{2(s+1)} I_{in} - \frac{I_0}{2(s+1)} = \frac{2s^2 + 5s + 4}{2(s+1)} A$$

$$(2) \quad A = \frac{2(s+1)}{2s^2 + 5s + 4} V_{in} + \frac{2s(s+1)}{2s(s+1)(2s^2 + 5s + 4)} I_{in} - \frac{I_0}{2s^2 + 5s + 4}$$

$$V_c(s) = \frac{2(s+1)}{2s^2 + 5s + 4} V_{in} + \frac{1.5}{2s^2 + 5s + 4} I_{in} - \frac{I_0}{2s^2 + 5s + 4}$$

$V_c$  zero-state

(1)

$V_c$  zero-input

(1)

Q-2

(a)  $H(j\omega) = \frac{10000 (j\omega 5)}{(j\omega + 100)(j\omega + 500)}$  (2)


(b)  $|H(j\omega)| = \frac{10000 \sqrt{\omega^2 + 5^2}}{\sqrt{\omega^2 + 100^2} \sqrt{\omega^2 + 500^2}}$  (2)

(c)  $|H(j\omega)|_{dB} = 20 \log \frac{10000 \sqrt{\omega^2 + 5^2}}{\sqrt{\omega^2 + 100^2} \sqrt{\omega^2 + 500^2}}$  (2)

(d)  $\angle H(j\omega) = \text{Tan}^{-1} \frac{\omega}{5} - \text{Tan}^{-1} \frac{\omega}{100} - \text{Tan}^{-1} \frac{\omega}{500}$  (3)

(e)  $|H(j\omega)| \Big|_{\omega=0} = \frac{10000 \cdot 5}{100 \cdot 500} = 1$       $|H(j\omega)|_{dB} \Big|_{\omega=0} = 20 \log 1 = 0$

asymptotes

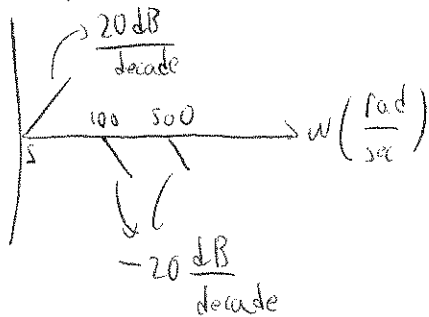


(1.1) \*  $0 < \omega < 5 \Rightarrow |H(j\omega)|_{dB} \approx 0$

(1.2) \*  $5 < \omega < 100 \Rightarrow |H(j\omega)|_{dB} = 0 + 20 \log \frac{\omega}{5}$

$\omega = 100 \Rightarrow |H(j\omega)|_{dB} = 20 \log 20$

(1.3) \*  $100 < \omega < 500 \Rightarrow |H(j\omega)|_{dB} = 20 \log 20$

(1.4) \*  $500 < \omega \Rightarrow |H(j\omega)|_{dB} = 20 \log 20 - 20 \log \frac{\omega}{500}$

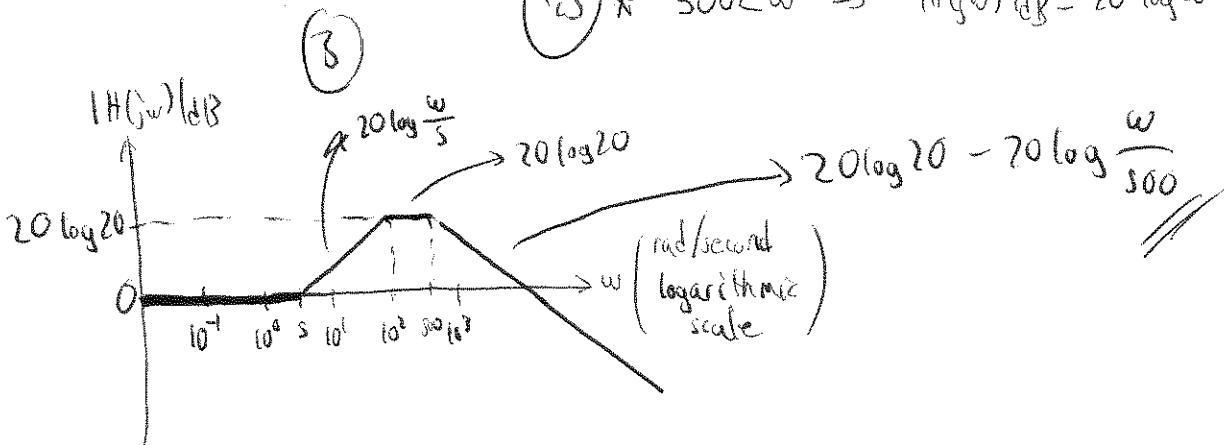


Q-2 (continue)

(f)  $\left. \frac{\angle H(j\omega)}{\omega} \right|_{\omega=0} = 0$

asymptotes

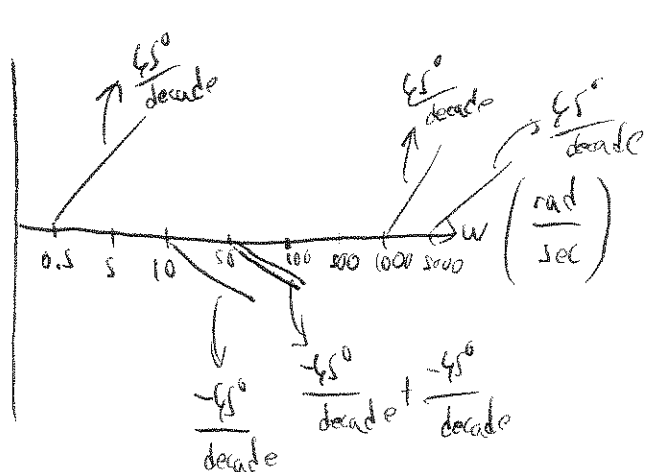
- $s = -5$  (zero)  $\omega = 5 \frac{\text{rad}}{\text{sec}}$ 
  - 0.5
  - 5
  - 50
- $s = -100$  (pole)  $\omega = 100 \frac{\text{rad}}{\text{sec}}$ 
  - 10
  - 100
  - 1000
- $s = -500$  (pole)  $\omega = 500 \frac{\text{rad}}{\text{sec}}$ 
  - 50
  - 500
  - 5000



- (1)  $0 < \omega < 0.5 \Rightarrow \angle H(j\omega) \approx 0$
- (1)  $0.5 < \omega < 10 \Rightarrow \angle H(j\omega) \approx 0 + 45 \log \frac{\omega}{0.5}$  if  $\omega = 10 \Rightarrow \angle H(j\omega) \approx 45 \log 20$
- (1)  $10 < \omega < 50 \Rightarrow \angle H(j\omega) \approx 45 \log 20$  (constant)
- (1)  $50 < \omega < 1000 \Rightarrow \angle H(j\omega) \approx 45 \log 20 - 90 \log \frac{\omega}{50}$   
 if  $\omega = 1000 \Rightarrow \angle H(j\omega) \approx 45 \log 20 - 90 \log \frac{1000}{50} = 45 \log 20 - 90 \log 20 = -45 \log 20$
- (1)  $1000 < \omega < 5000 \Rightarrow \angle H(j\omega) \approx -45 \log 20 - 45 \log \frac{\omega}{1000}$

if  $\omega = 5000 \Rightarrow \angle H(j\omega) \approx -45 \log 20 - 45 \log 5 = -90^\circ$

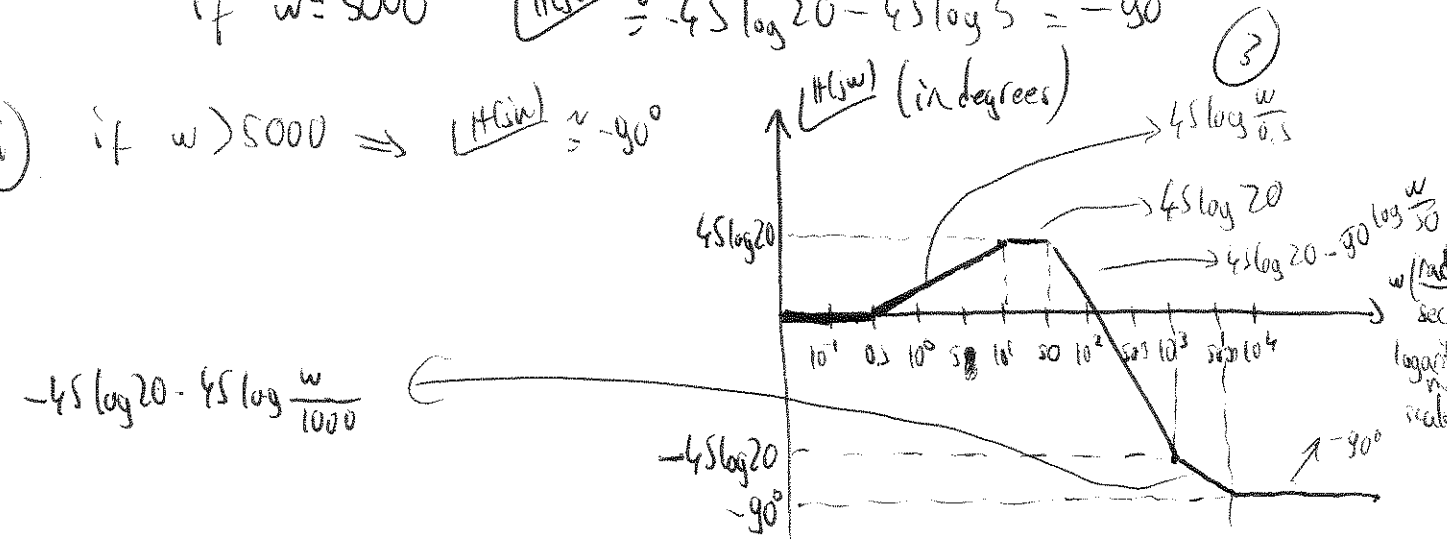- (1) if  $\omega > 5000 \Rightarrow \angle H(j\omega) \approx -90^\circ$



Q-3 -  $H(s) = \frac{10100s}{(s+100)(s+10000)}$

$H(j\omega) = \frac{10100j\omega}{(j\omega+100)(j\omega+10000)}$

$|H(j\omega)| = \frac{10100\omega}{\sqrt{\omega^2+100^2} \sqrt{\omega^2+(10000)^2}}$

or  $|H(j\omega)| = \frac{10100\omega}{\sqrt{(10^6 - \omega^2)^2 + (10100\omega)^2}}$

(a)

$|H(j\omega)|$  is maximized when  $\omega^2 = 10^6$   $\omega = 1000 \frac{\text{rad}}{\text{second}} = \omega_0$   
 (4)  $\downarrow$   
 resonant frequency

(b)

$|H(j\omega)|_{\max} = |H(j\omega)| \Big|_{\omega = \omega_0 = 1000 \frac{\text{rad}}{\text{second}}} = \frac{10100 \cdot 1000}{10100 \cdot 1000} = 1 //$

at the half power frequencies

$|H(j\omega)| \Big|_{\omega = \omega_c} = \frac{|H(j\omega)|_{\max}}{\sqrt{2}} = \frac{1}{\sqrt{2}} = \frac{10100\omega_c}{\sqrt{(\omega_c^2+100^2)(\omega_c^2+10000^2)}} = \frac{1}{\sqrt{2}}$  (2)

$2 \cdot 10100^2 \omega_c^2 = (\omega_c^2 + 100^2)(\omega_c^2 + 10000^2)$   $\omega_c^2 = x$

$2 \cdot 10100^2 x = (x + 100^2)(x + 10000^2)$

$2 \cdot (10100^2) x = (x + 100^2)(x + 10000^2)$

~~$2 \cdot 10100^2 x = (x + 100^2)(x + 10000^2)$~~

$2 \cdot (10100)^2 x = x^2 + (10000^2 + 100^2)x + 10^{12}$   
 $= (x - 100^2)(x - 10000^2)$  (2)

$x = 100^2$   $\omega_{c1} = 100 \frac{\text{rad}}{\text{sec}}$  (0.5)  
 $x = 10000^2$   $\omega_{c2} = 10000 \frac{\text{rad}}{\text{sec}}$  (0.5)

Q-4-

(3)

$$Y(s) = \frac{5}{(s^2+1)(s^2+2s+2)} = \frac{As+B}{s^2+1} + \frac{Cs+D}{s^2+2s+2}$$

$$(2) \quad 5 = (As+B)(s^2+2s+2) + (Cs+D)(s^2+1)$$

$$5 = As^3 + (2A+B)s^2 + (2A+2B)s + 2B + Cs^3 + Ds^2 + Cs + D$$

$$5 = (A+C)s^3 + (2A+B+D)s^2 + (2A+2B+C)s + 2B+D$$

$$A+C=0 \quad 2A+B+D=0 \quad 2A+2B+C=0 \quad 2B+D=5$$

$$A = -C$$

$$-2C + \frac{C}{2} + D = 0$$

$$-\frac{3C}{2} + D = 0$$

$$D = \frac{3C}{2}$$

$$-2C + 2B + C = 0$$

$$B = \frac{C}{2}$$

$$C + \frac{3C}{2} = 5$$

$$\frac{5C}{2} = 5 \quad C=2$$

$$B=1 \quad (2)$$

$$D=3$$

$$A=-2$$

$$Y(s) = \frac{-2s+1}{s^2+1} + \frac{2s+3}{s^2+2s+2} = -2 \frac{s}{s^2+1} + 1 \frac{1}{s^2+1} + 2 \frac{(s+1)}{(s+1)^2+1^2} + 1 \frac{1}{(s+1)^2+1^2}$$

$\downarrow \mathcal{L}^{-1}$

$$y(t) = [2 \cos(t) + \sin(t) + 2e^{-t} \cos(t) + e^{-t} \sin(t)] u(t)$$

Q-5- The sources have the same input angular frequencies ( $\omega = 2 \frac{\text{rad}}{\text{second}}$ )

In Phasor domain


$$V_{in}(t) = \frac{\sqrt{65}}{8} \cos(2t - \theta_1) \rightarrow \bar{V}_{in} = \frac{\sqrt{65}}{8} e^{-j\theta_1} = \frac{\sqrt{65}}{8} [\cos \theta_1 - j \sin \theta_1]$$



$$= \frac{\sqrt{65}}{8} \left[ \frac{7}{\sqrt{65}} - j \frac{4}{\sqrt{65}} \right]$$

$$\textcircled{2} = \frac{7}{8} - \frac{4j}{8} \text{ Volt}$$
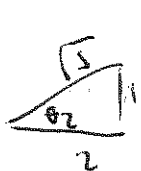
$$I_{in}(t) = \frac{\sqrt{5}}{2} \cos(2t + \theta_2) \rightarrow \bar{I}_{in} = \frac{\sqrt{5}}{2} e^{j\theta_2} = \frac{\sqrt{5}}{2} \left[ \frac{2}{\sqrt{5}} + j \frac{1}{\sqrt{5}} \right]$$



$$\cos \theta_2 = \frac{2}{\sqrt{5}} \quad \sin \theta_2 = \frac{1}{\sqrt{5}}$$

$$\textcircled{2} = 1 + \frac{j}{2} \text{ Amper}$$


The circuit in phasor domain

$$X_{R_1} = X_{R_2} = R_1 = R_2 = 1 \Omega \quad \textcircled{1}$$

$$X_C = \frac{1}{j\omega C} = \frac{1}{j \times 2 \times 2} = \frac{1}{4j} \Omega \quad \textcircled{1}$$

$$X_L = j\omega L = j \times 2 \times 1 = 2j \Omega \quad \textcircled{1}$$

Circuit in phasor domain

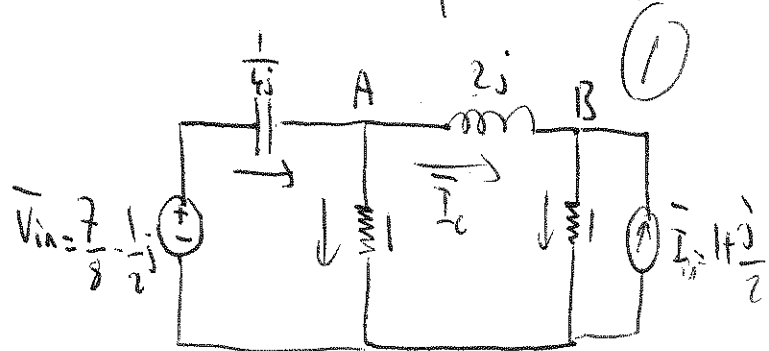

$$\frac{\bar{V}_{in} - A}{\frac{1}{4j}} = \frac{A}{1} + \frac{A-B}{2j} \quad \textcircled{2}$$

$$\frac{A-B}{2j} + 1 + \frac{j}{2} = \frac{B}{1} \quad \textcircled{2}$$

$$A = 2 \text{ V} \quad \textcircled{2}$$

$$B = 1 \text{ V} \quad \textcircled{2}$$



$$\textcircled{a} \bar{I}_L = \frac{2-1}{2j} = \frac{1}{2j} = \frac{1}{2} \cdot \frac{1}{j} = \frac{1}{2} (-j) = \frac{1}{2} e^{-j90^\circ} \quad \textcircled{1}$$

$$\textcircled{1} \bar{I}_L(t) = \frac{1}{2} \cos(2t - 90^\circ) = \frac{1}{2} \sin(2t) \text{ Amper} //$$

$$\textcircled{b} P_{R_1} = \frac{1}{2} \bar{I}_{R_1} \bar{I}_{R_1} R_1 = \frac{1}{2} \left( \frac{2-0}{R_1} \right) \cdot \left( \frac{2-0}{R_1} \right)^* R_1 = \frac{1}{2} \times \frac{4}{R_1} = 2 \text{ Watt} //$$

Q-6 - Frequencies are different  $\omega_1 = 1 \frac{\text{rad}}{\text{sec}}$   $\omega_2 = 2 \frac{\text{rad}}{\text{second}}$

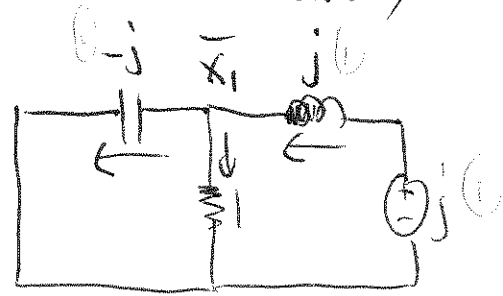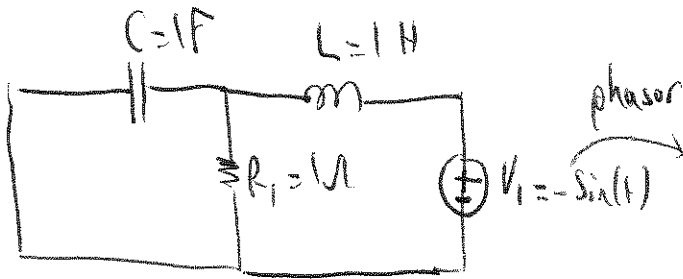Kill  $V_2$  (short  $V_2$ ) (input frequency for  $V_1(t)$  is  $\omega_1 = 1 \frac{\text{rad}}{\text{second}}$ )



$V_1 = -\sin(t) \rightarrow V_1 = \cos(t+90^\circ) \xrightarrow{\text{phasor}} \vec{V}_1 = 1 \angle 90^\circ = j \text{ Volt}$

$X_R = 1 \Omega$

$X_L = j\omega_1 L = j \cdot 1 \cdot 1 = j$

$X_C = \frac{1}{j\omega_1 C} = \frac{1}{j \cdot 1 \cdot 1} = -j$


$\frac{j - X_1}{j} = \frac{X_1}{1} + \frac{X_1}{j}$  (1)

$1 = \frac{X_1}{j} + X_1 - \frac{X_1}{j}$

$1 = X_1$


$\rightarrow X_1(t) = \cos(t)$

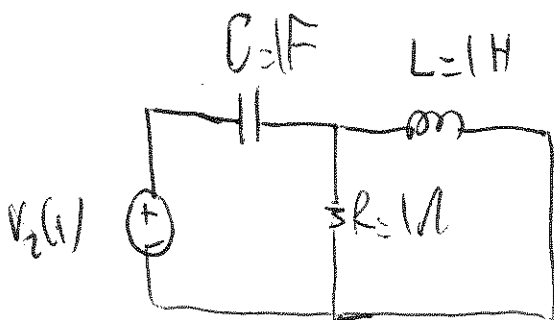Kill  $V_1$  (input frequency for  $V_2(t)$  is  $\omega_2 = 2 \frac{\text{rad}}{\text{second}}$ ) (short  $V_1$ )




phasor

$\vec{V}_2 = \frac{1}{2} + j\frac{3}{4}$

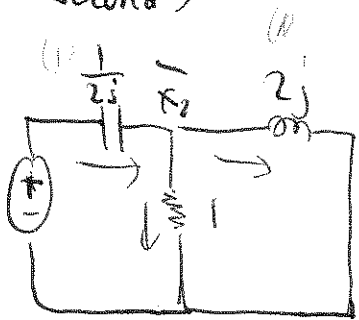

$V_2 = \frac{\sqrt{13}}{4} \cos(2t + \theta_2) \xrightarrow{\text{phasor}} \frac{\sqrt{13}}{4} (\cos\theta_2 + j\sin\theta_2)$

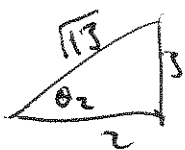$= \frac{\sqrt{13}}{4} \left[ \frac{2}{\sqrt{13}} + j\frac{3}{\sqrt{13}} \right]$



$\vec{V}_2 = \frac{1}{2} + j\frac{3}{4} \text{ Volt}$

$\frac{\vec{V}_2 - X_2}{\frac{1}{2j}} = \frac{X_2}{1} + \frac{X_2}{2j}$

$\frac{\frac{1}{2} + j\frac{3}{4} - X_2}{\frac{1}{2j}} = \frac{X_2}{1} + \frac{X_2}{2j}$

$X_{R1} = 1$

$X_L = j\omega_2 L = 2j$

$X_C = \frac{1}{j\omega_2 C} = \frac{1}{2j}$

✓



Q-6- continue

$$j + \left(\frac{j^2}{2}\right) - 2j\bar{X}_2 = \bar{X}_2 + \frac{\bar{X}_2}{2j}$$

$$j - \frac{3}{2} = \bar{X}_2 \left[1 + \frac{1}{2j} + 2j\right]$$

$$j - \frac{3}{2} = \bar{X}_2 \left[1 + \frac{3}{2}j\right]$$



$$\bar{X}_2 = j \rightarrow X_2(t) = \cos(2t + 90^\circ) = e^{j90}$$

(a) At SSS (Sinusoidal Steady State)

$$A = X_1(t) + X_2(t) = \cos(t) + \cos(2t + 90^\circ) = \cos(t) - \sin(2t) \text{ Volt}$$

$$I_R = \frac{A}{R_1} = \frac{\cos(t) - \sin(2t)}{1} = \cos(t) - \sin(2t) \text{ Amper}$$

$$\begin{aligned} (b) P_{R_1, SSS} &= \frac{1}{2} \frac{\bar{X}_1 \bar{X}_1^*}{R_1} + \frac{1}{2} \frac{\bar{X}_2 \bar{X}_2^*}{R_1} \\ &= \frac{1}{2} \frac{1 \cdot 1}{1} + \frac{1}{2} \frac{(j) \cdot (-j)}{1} = \frac{1}{2} + \frac{1}{2} = 1 \text{ Watt} \end{aligned}$$