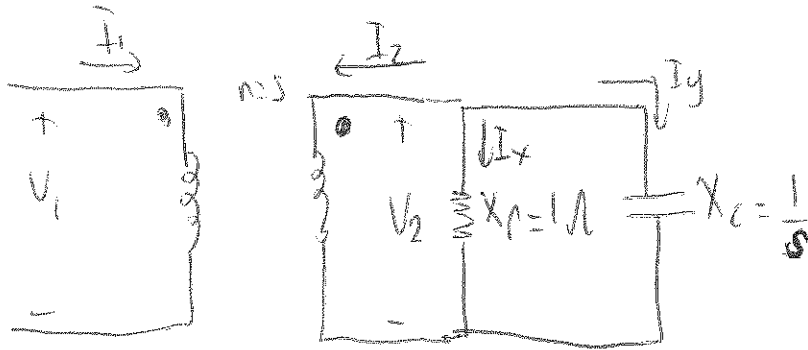


ECE 232 - Example Questions

Q-1

$$V_1 = 5V_2$$

$$I_2 = -5I_1$$



$$V_1 = 5V_2$$

$$I_x = \frac{V_2}{X_1}$$

$$I_y = \frac{V_2}{X_c}$$

$$I_x + I_y = -I_2$$

$$\frac{V_2}{1} + \frac{V_2}{\frac{1}{s}} = -I_2$$

$$I_x = \frac{V_2}{1}$$

$$I_y = \frac{V_2}{\frac{1}{s}}$$

$$V_2 [1 + s] = -I_2$$

$$V_2 = \frac{-I_2}{1+s}$$

$$V_1 = 5V_2 = 5 \frac{-I_2}{1+s}$$

$$I_2 = -5I_1$$

$$V_1 = 5 \frac{-I_2}{1+s}$$


↓

$$V_1 = 5 \frac{-(-5I_1)}{1+s}$$


$$V_1 = \frac{25I_1}{1+s}$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{25}{1+s}$$


Q-2-

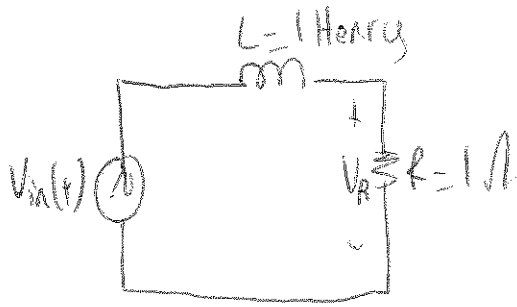

$u(t) \rightarrow$ unit step input

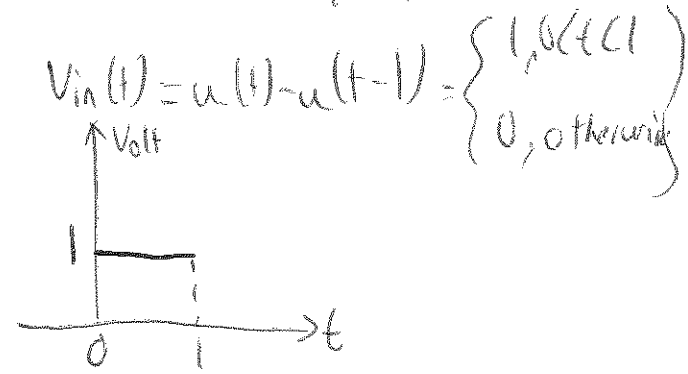

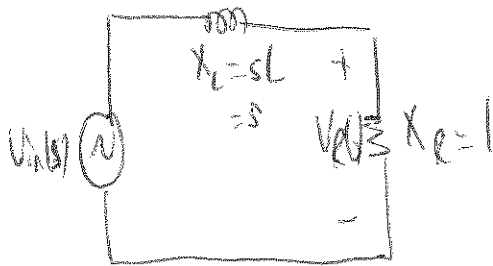(a) The impulse response (in Laplace domain)



$$V_R(s) = \frac{1}{1+s} V_{in}(s)$$



$$\frac{V_R(s)}{V_{in}(s)} = H(s) = \frac{1}{1+s} \rightarrow \text{transfer function}$$

$$h(t) = \mathcal{L}^{-1}\{H(s)\} = \mathcal{L}^{-1}\left\{\frac{1}{1+s}\right\} = e^{-t} u(t)$$

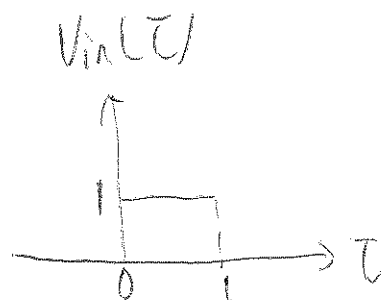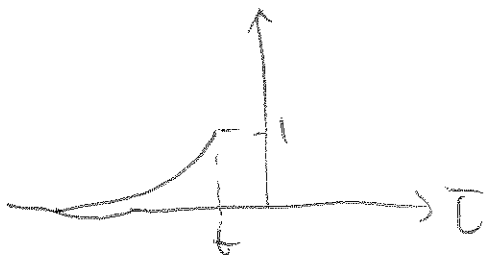
(b) Convolution integral

$$V_R(t) = \int_{-\infty}^t V_{in}(t-\tau) h(\tau) d\tau = \int_{-\infty}^t V_{in}(\tau) h(t-\tau) d\tau$$

$$h(t-\tau) = e^{-(t-\tau)} u(t-\tau) \quad \left\{ \begin{array}{l} t \text{ parameter} \\ \tau \text{ variable} \end{array} \right.$$




if $t < 0$

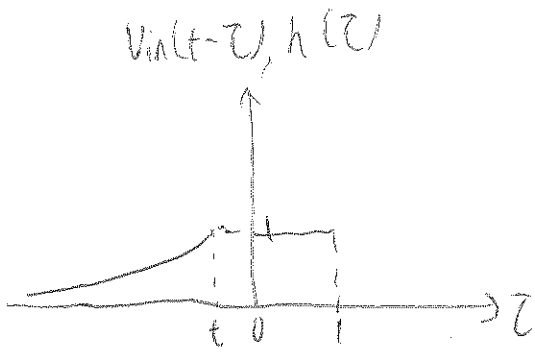

$$y(t) = \int_{-\infty}^t v_{in}(t-\tau) h(\tau) d\tau = \int_{-\infty}^t v_{in}(\tau) h(t-\tau) d\tau = 0$$

if $0 < t < 1$

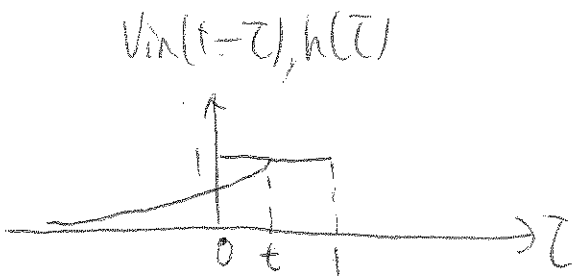


$$y(t) = \int_{-\infty}^t v_{in}(\tau) h(t-\tau) d\tau = \int_{-\infty}^0 0 d\tau + \int_0^t e^{-(t-\tau)} \cdot 1 d\tau$$

$$\begin{aligned} &= \int_0^t e^{-(t-\tau)} d\tau = e^{-t} \int_0^t e^{\tau} d\tau = e^{-t} \left[\frac{e^{\tau}}{1} \right]_0^t \\ &= e^{-t} [e^t - 1] = 1 - e^{-t} \end{aligned}$$


↑
t is just a variable

if $1 < t$

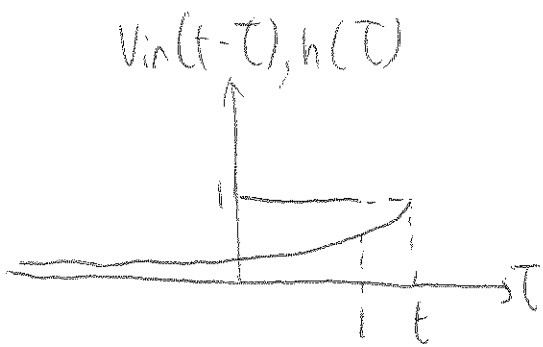

$$\begin{aligned} y(t) &= \int_{-\infty}^t v_{in}(\tau) h(t-\tau) d\tau \\ &= \int_{-\infty}^0 0 d\tau + \int_0^1 e^{-(t-\tau)} \cdot 1 d\tau + \int_1^t 0 d\tau \\ &= \int_0^1 e^{-(t-\tau)} d\tau = e^{-t} \int_0^1 e^{\tau} d\tau \\ &= e^{-t} [e^{\tau}]_0^1 = e^{-t} [e^1 - 1] \end{aligned}$$

Q-3

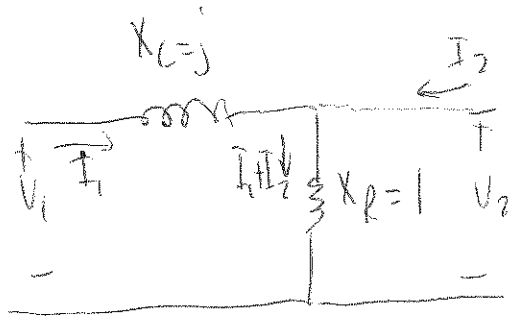

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_1 = j(I_1) + 1(I_1 + I_2)$$

$$V_2 = 1(I_1 + I_2)$$

$$V_1 = (j+1)I_1 + I_2$$


$$V_2 = I_1 + I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j+1 & 1 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$A = j+1 \quad B = 1$$

$$C = 1 \quad D = 1$$

Q-4

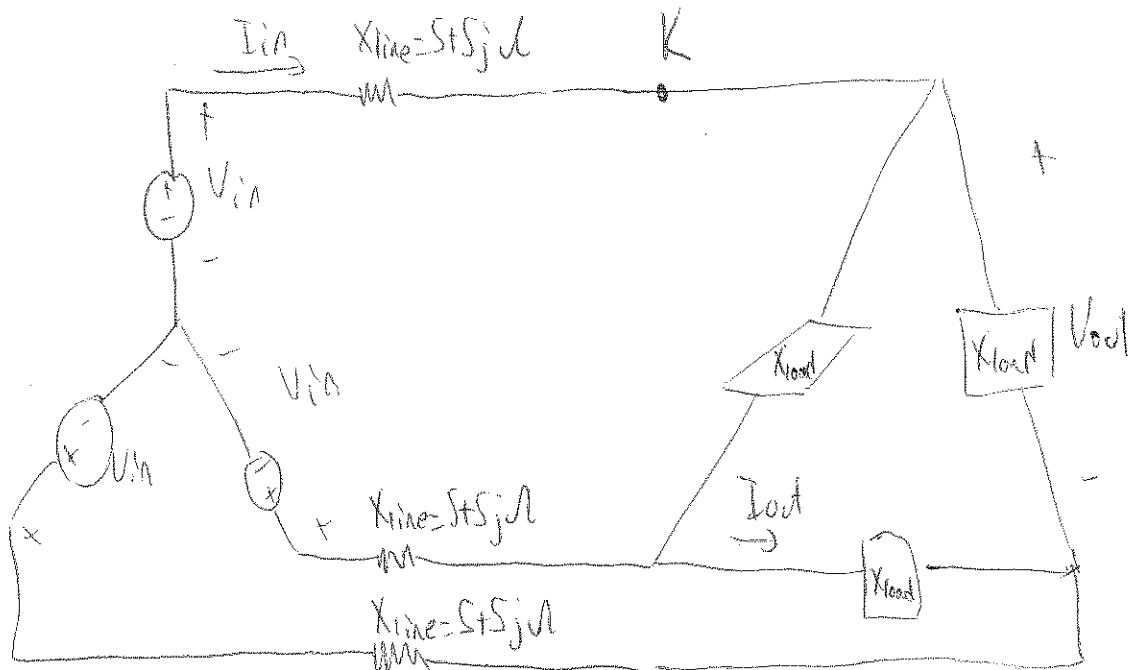

$$P_T = 100 \text{ Watt}$$

$$Q_T = -100 \text{ VAR}$$

$$|S_T| = \sqrt{P_T^2 + Q_T^2} = 100\sqrt{2} \text{ VA}$$

complex power

$$|S_T| = |V_{Ln}| |I_{Ln}| \sqrt{3} \Rightarrow 100\sqrt{2} = 100\sqrt{3} |I_{Ln}| \quad |I_{Ln}| = \frac{\sqrt{2}}{\sqrt{3}} \text{ Amper}$$

$$P_{\text{Line}} = 3 \operatorname{Re}\{X_{\text{line}}\} |I_{Ln}|^2 = 3 \times 5 \times \left(\frac{\sqrt{2}}{\sqrt{3}}\right)^2 = \frac{3 \times 5 \times 2}{3} = 10 \text{ Watt}$$

$$Q_{\text{Line}} = 3 \operatorname{Im}\{X_{\text{line}}\} |I_{Ln}|^2 = 3 \times 5 \times \left(\frac{\sqrt{2}}{\sqrt{3}}\right)^2 = 10 \text{ VAR}$$

average power at K $\leftarrow P_K = P_T - P_{\text{Line}} = 100 - 10 = 90 \text{ Watt}$

reactive power at K $\leftarrow Q_K = Q_T - Q_{\text{Line}} = -100 - 10 = -110 \text{ Watt}$

$$\begin{aligned} |S_K| &= \sqrt{P_K^2 + Q_K^2} \\ &= \sqrt{90^2 + (-110)^2} \\ &= \sqrt{(81 + 121) 10^2} \\ &= \sqrt{222} 10 \text{ VA} \end{aligned}$$

$$|S_K| = |S_{Load}| = 3|I_{out}| |V_{out}| = \sqrt{3} |I_{in}| |V_{out}|$$

$$\sqrt{222} \cdot 10 = \sqrt{3} \frac{\sqrt{2}}{\sqrt{3}} |V_{out}| \quad |V_{out}| = \sqrt{111} \cdot 10 \text{ (rms)}$$

$$|I_{out}| = \frac{|I_{in}|}{\sqrt{3}} = \frac{\sqrt{2}}{\sqrt{3}} \frac{1}{\sqrt{3}} = \frac{\sqrt{2}}{3} \text{ Amper / (rms)}$$

~~(S)~~ $S_K = 90 - 110j \text{ VA}$

$$S_K = 3V_{out} \bar{I}_{out}^* = 3(X_{Load} I_{out}) \bar{I}_{out}^* = 3|I_{out}|^2 X_{Load}$$

$$90 - 110j = 3 \frac{2}{3} X_{Load}, \quad \frac{90 - 110j}{2} = X_{Load} = 45 - 55j \text{ VA}$$