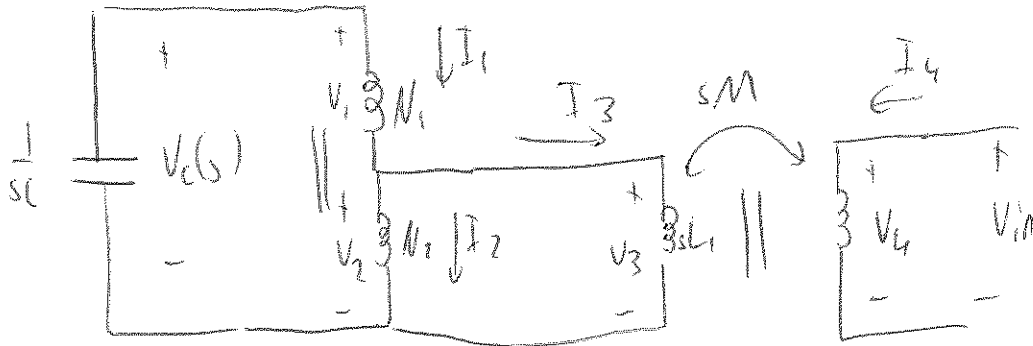


ECE 232 Homework 3

Q-1 In Laplace domain



in Laplace domain

$$\begin{aligned} V_3 &= sL_1 I_3 + sM I_4 \\ V_4 &= sM I_3 + sL_2 I_4 \\ V_1 &= \frac{N_1}{N_2} V_2 \\ I_1 &= -\frac{N_2}{N_1} I_2 \end{aligned}$$

$$V_c = -I_1 \frac{1}{sC} \quad I_3 = I_1 - I_2 = I_1 - \left(-\frac{N_1}{N_2}\right) I_1 = \left(1 + \frac{N_1}{N_2}\right) I_1$$

$$V_{in} = V_4 = sM I_3 + sL_2 I_4$$

$$V_{in} = V_4 = sM \left(1 + \frac{N_1}{N_2}\right) I_1 + sL_2 I_4$$

$$V_3 = V_2 = V_c - V_1$$

$$V_2 = V_c - \frac{N_1}{N_2} V_2$$

$$\left(1 + \frac{N_1}{N_2}\right) V_2 = V_c$$

$$\frac{N_1 + N_2}{N_2} V_2 = V_c$$

$$\begin{aligned} V_3 &= sL_1 I_3 + sM I_4 \\ \frac{N_2}{N_1 + N_2} V_c &= sL_1 \left(\frac{N_2 + N_1}{N_2}\right) I_1 + sM I_4 \end{aligned}$$

$$V_2 = V_3 = \frac{N_2}{N_1 + N_2} V_c$$

Q-1 (continue)

$$V_{in} - sM \left(1 + \frac{N_1}{N_2} \right) I_1$$

$$\frac{N_2}{N_1 + N_2} V_C - sL_1 \left(\frac{N_2 + N_1}{N_2} \right) I_1$$

$$\frac{V_{in} - sM \left(1 + \frac{N_1}{N_2} \right) I_1}{sL_2} = \frac{\frac{N_2}{N_1 + N_2} V_C - sL_1 \left(\frac{N_2 + N_1}{N_2} \right) I_1}{sM} = I_1$$

$$sM V_{in} - s^2 M^2 \left(\frac{N_1 + N_2}{N_2} \right) I_1 = \frac{N_2 s L_2}{N_1 + N_2} V_C - s^2 L_1 L_2 \left(\frac{N_2 + N_1}{N_2} \right) I_1$$

$$sM V_{in} = \frac{sL_2 N_2}{N_1 + N_2} V_C + (s^2 M^2 - s^2 L_1 L_2) \left(\frac{N_1 + N_2}{N_2} \right) I_1$$

$$I_1 = -V_C s C$$

$$sM V_{in} = \frac{sL_2 N_2}{N_1 + N_2} V_C + (s^2 L_1 L_2 - s^2 M^2) s C \left(\frac{N_1 + N_2}{N_2} \right) V_C$$

$$sM V_{in} = \left[\frac{sL_2 N_2^2}{(N_1 + N_2) N_2} + \frac{(s^2 L_1 L_2 - s^2 M^2) (N_1^2 + N_2^2) s C}{(N_1 + N_2) N_2} \right] V_C$$

$$\frac{V_C}{V_{in}} = \frac{sM N_2 (N_1 + N_2)}{s \left[(s^2 L_1 L_2 - s^2 M^2) (N_1^2 + N_2^2) C + N_2^2 L_2 \right]}$$

$$\frac{V_C}{V_{in}} = \frac{M(N_2)(N_1 + N_2)}{s^2 (L_1 L_2 - M^2) (N_1^2 + N_2^2) C + N_2^2 L_2}$$

Q-2

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

* $A = \frac{V_1}{V_2} \Big|_{-I_2=0}$

$$I_2 = 0 = g_{21} V_1 + g_{22} V_2$$

$$\hookrightarrow \frac{V_1}{V_2} = -\frac{g_{22}}{g_{21}} = A$$

* $C = \frac{I_1}{V_2} \Big|_{-I_2=0}$

$$I_1 = g_{11} V_1 + g_{12} V_2$$

$$\frac{I_1}{V_2} = g_{11} \left(\frac{V_1}{V_2} \right) + g_{12} \frac{V_2}{V_2}$$

$$\frac{I_1}{V_2} = g_{11} \left(-\frac{g_{22}}{g_{21}} \right) + g_{12}$$

$$\frac{I_1}{V_2} = C = g_{12} - \frac{g_{11} g_{22}}{g_{21}}$$

* $B = \frac{V_1}{-I_2} \Big|_{V_2=0}$

$$I_1 = g_{11} V_1 + g_{12} V_2$$

$$I_2 = g_{21} V_1 + g_{22} V_2$$

if $V_2 = 0$ $I_1 = g_{11} V_1$
 $I_2 = g_{21} V_1$

$$B = -\frac{V_1}{I_2} = -\frac{1}{g_{21}}$$

* $D = \frac{I_1}{-I_2} \Big|_{V_2=0} = -\frac{g_{11}}{g_{21}}$