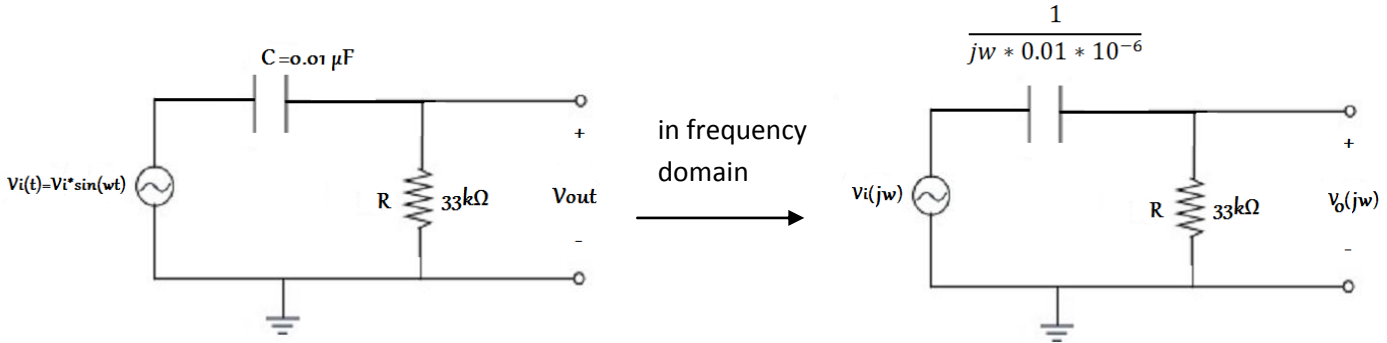


Ece 322 - Advanced Electrical Circuit Analysis Lab Manual 5

Frequency Response



$$1. \quad H(jw) = \frac{V_o(jw)}{V_i(jw)} = \frac{33 \cdot 10^3}{33 \cdot 10^3 - \frac{10^8}{w}} = \frac{33 \cdot 10^3 w}{33 \cdot 10^3 w - 10^8 j}$$

(if $w = 0$ $|H(jw)| = 0$, if $w = \infty$ $|H(jw)| = 1$) : high - pass filter

$$\text{Magnitude } (|H(jw)|)_{max} = 1$$

$$|H(jw)| = \frac{33 \cdot 10^3 w}{\sqrt{(33 \cdot 10^3 w)^2 + 10^{16}}}$$

For corner frequency (half power frequency)

$$|H(jw_c)| = \frac{1}{\sqrt{2}} |H(jw)|_{max}$$

$$\frac{(33 \cdot 10^3 \cdot w_c)^2}{33^2 \cdot 10^6 \cdot w_c^2 + 10^{16}} = \frac{1}{2}$$



$$w_c^2 = \frac{10^{16}}{33^2 \cdot 10^6}$$

$$w_c = \frac{10^5}{33} \cong 3030 \text{ rad/sec} \quad f_c = \frac{3030}{2\pi} = 483 \text{ Hertz}$$


phase

$$H(jw) = \frac{33 \cdot 10^3 w}{33 \cdot 10^3 w - 10^8 j} = \frac{33 \cdot 10^3 w \cdot (33 \cdot 10^3 w + 10^8 j)}{33^2 \cdot 10^6 w^2 + 10^{16}}$$
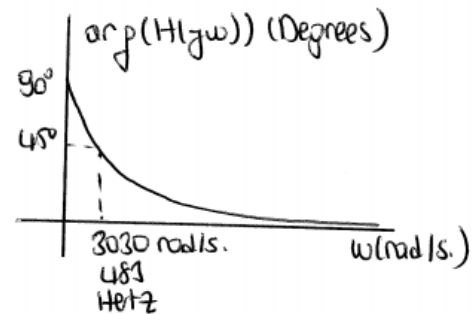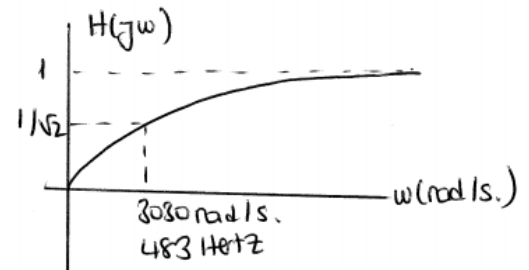
$$\arg(H(jw)) = \tan^{-1}\left(\frac{10^8}{33 \cdot 10^3 w}\right)$$




2.

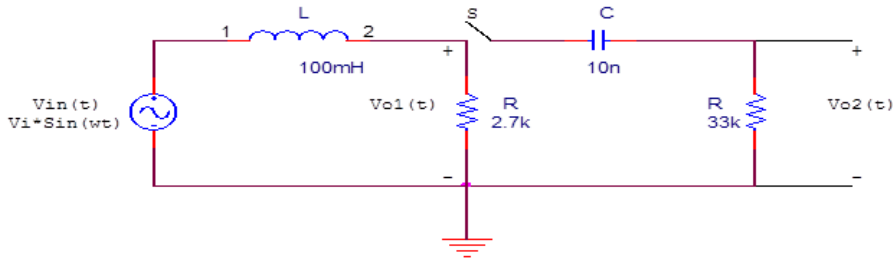

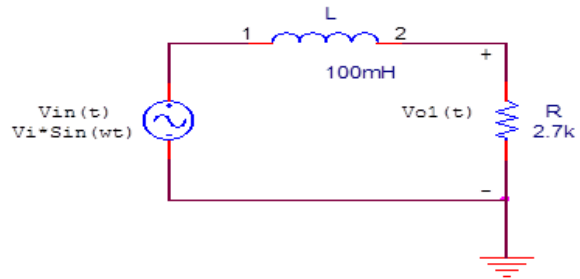a. S is open
in phasor domain

$$H_1(j\omega) = \frac{V_{o1}(j\omega)}{V_i(j\omega)} = \frac{2700}{2700 + 0.1j\omega}$$



(if $\omega = 0$ $|H(j\omega)| = 1$, if $\omega = \infty$ $|H(j\omega)| = 0$) : low - pass filter


Magnitude $(|H_1(j\omega)|)_{max} = 1$

$$|H_1(j\omega)| = \frac{2700}{\sqrt{2700^2 + 0.1^2\omega^2}}$$

phase

$$H_1(j\omega) = \frac{2700 * (2700 - 0.1j\omega)}{2700^2 + 0.1^2\omega^2}$$
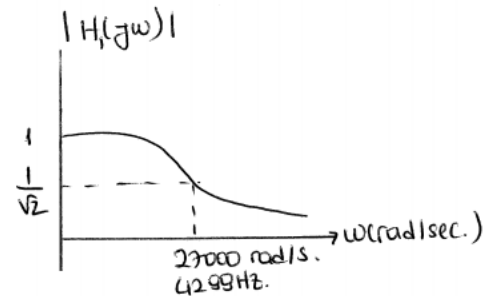
$$\arg(H(j\omega)) = \tan^{-1}\left(\frac{-0.1\omega}{2700}\right) = \tan^{-1}\left(\frac{-\omega}{27000}\right)$$




For half-power frequency ω_c

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |H(j\omega)|_{max}$$



$$\frac{2700^2}{2700^2 * (0.1\omega_c)^2} = \frac{1}{2}$$

$$\omega_c = 27000 \text{ rad/sec}$$
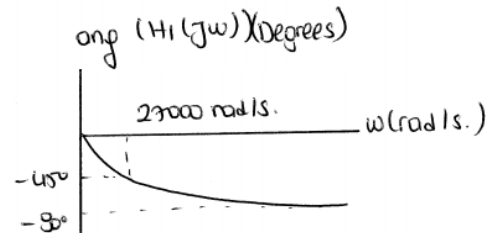
$$f_c = \frac{27000}{2\pi} = 4299 \text{ Hertz}$$



b.

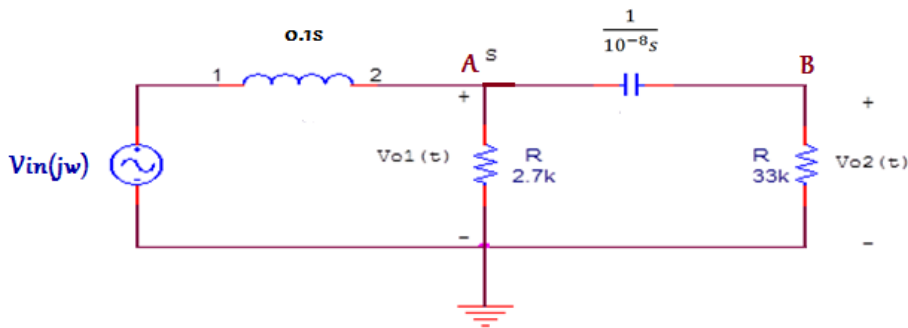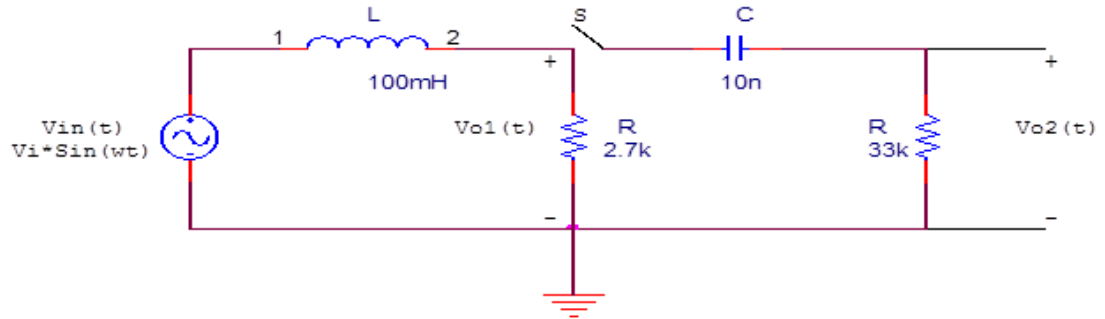

$$\frac{V_i - A}{0.1s} = \frac{A}{2700} + \frac{As}{10^8 + 33000s}$$

$$V_i = A \left(\frac{27 * 10^9 + 991 * 10^4 s + 357s^2}{27 * 10^9 + 891 * 10^4 s} \right)$$

$$\frac{A}{\frac{10^8}{s} + 33000} = \frac{B}{33000}$$

$$A = B \frac{33s + 10^5}{33s}$$

$$V_i = B \frac{33s + 10^5}{33s} \left(\frac{27 * 10^9 + 991 * 10^4 s + 357s^2}{27 * 10^9 + 891 * 10^4 s} \right)$$

$$B = V_{o2}$$

$$V_i = V_{o2} \frac{33s + 10^5}{33s} \left(\frac{27 * 10^9 + 991 * 10^4 s + 357s^2}{27 * 10^4 (33s + 10^5)} \right)$$

$$\frac{V_{o2}}{V_i} = H_2(s) = \frac{33 * 27 * 10^4 * s}{27 * 10^9 + 991 * 10^4 s + 357s^2}$$

$$H_2(jw) = \frac{891 * 10^4 * jw}{27 * 10^9 + 991 * 10^4 jw - 357w^2}$$

Magnitude response

$$|H_2(jw)| = \frac{891 * 10^4 * w}{\sqrt{991^2 * 10^8 w^2 + (27 * 10^9 - 357w^2)^2}}$$

Phase response

$$H_2(j\omega) = \frac{891 * 10^4 * j\omega}{27 * 10^9 + 991 * 10^4 j\omega - 357\omega^2}$$

by multiplying by conjugate

$$\text{Arg}(H_2(j\omega)) = \tan^{-1} \frac{27 * 10^9 \omega - 357\omega^3}{991 * 10^4 * \omega^2} = \tan^{-1} \frac{27 * 10^9 - 357\omega^2}{991 * 10^4 * \omega}$$

For resonant angular frequency the imaginary part of the response must be zero

$$H_2(j\omega) = \frac{891 * 10^4 * [(27 * 10^9 \omega - 357\omega^3)j + 991 * 10^4 \omega^2]}{(27 * 10^9 - 357\omega^2)^2 + (991 * 10^4 \omega)^2}$$

$$27 * 10^9 \omega - 357\omega^3 = 0$$

$$\omega = 0 \quad \text{or}$$

$$\omega^2 = \frac{27 * 10^9}{357}$$

$$\omega = \sqrt{\frac{27 * 10^9}{357}} = 0.8697 * 10^4 = 8697 \frac{\text{rad}}{\text{sec}} = 1385 \text{Hertz}$$

The magnitude at the resonant angular frequency

$$H_2(j\omega) = \frac{891 * 10^4 * \left[\left(\frac{27 * 10^9}{357} \right) * 991 * 10^4 \right]}{\left(\frac{27 * 10^9}{357} \right) * (991 * 10^4)^2} = \frac{891}{991} = 0.899$$

When does $|H_2(j\omega)|$ reaches its maximum value

$$\frac{d}{d\omega} |H_2(j\omega)| = \frac{891 * 10^4 * [-2 * 127449\omega^4 + 2 * 729 * 10^{18}]}{2(127449\omega^4 + 789301 * 10^8 \omega^2 + 729 * 10^{16})} = 0$$

$$\omega^4 = 2 * \frac{729 * 10^{18}}{2 * 127449}$$

$$\omega^2 = \frac{27 * 10^9}{357}$$

$$\omega \cong \frac{8697 \text{rad}}{\text{sec}} = 1385 \text{Hertz}$$

These results indicates that the max value for $|H_2(j\omega)|$, obtained when the circuit is operating in the resonant frequency. $\text{arg}(|H_2(j\omega)|)_{\text{max}} = \omega_{\text{resonant-frequency}}$

$$|H_2(j\omega)| = 1 \quad \text{This value is not possible since } (|H_2(j\omega)|)_{\text{max}} = 0.89$$

To find the corner frequencies (half-power frequencies) find the frequencies where phase = $\mp 45^\circ$

First corner frequency

$$\tan^{-1} \frac{27 * 10^9 - 357w^2}{991 * 10^4 * w} = 45^\circ$$

$$1 = \frac{27 * 10^9 - 357w^2}{991 * 10^4 * w}$$

$$0 = 357w^2 + 991 * 10^4 * w - 27 * 10^9$$

$$w_{1,2} = \frac{-991 * 10^4 \mp \sqrt{(991 * 10^4)^2 + 4 * 357 * 27 * 10^9}}{2 * 357} = 0.2499 * 10^4 = \frac{2499 \text{ rad}}{\text{sec}} = 398 \text{ Hertz}$$

Second corner frequency

$$\tan^{-1} \frac{27 * 10^9 - 357w^2}{991 * 10^4 * w} = -45^\circ$$

$$-1 = \frac{27 * 10^9 - 357w^2}{991 * 10^4 * w}$$

$$0 = 357w^2 - 991 * 10^4 * w - 27 * 10^9$$

$$w_{1,2} = \frac{991 * 10^4 \mp \sqrt{(991 * 10^4)^2 + 4 * 357 * 27 * 10^9}}{2 * 357} = 30259 \text{ rad/sec} = 4818 \text{ Hertz}$$

$|H_2(jw)|$ at corner frequencies

$$H_2(jw) = \frac{891 * 10^4 * 991 * 10^4 w^2 \left[\frac{(27 * 10^9 w - 357w^3)}{991 * 10^4 w^2} j + 1 \right]}{(991 * 10^4 w)^2 \left(1 + \frac{27 * 10^9 - 357w^2}{991 * 10^4 w} \right)^2}$$

at w_{c1} $\frac{27 * 10^9 - 357w^2}{991 * 10^4 * w} = 1$



at w_{c2} $\frac{27 * 10^9 - 357w^2}{991 * 10^4 * w} = -1$

$$H_2(w_{c1}) = \frac{891}{991} * \frac{1+j}{1+1^2} = \frac{891}{991} * \frac{1+j}{2}$$

$$H_2(w_{c2}) = \frac{891}{991} * \frac{1-j}{1+1^2} = \frac{891}{991} * \frac{1-j}{2}$$

$$|H_2(w_{c1})| = \frac{891}{991} * \frac{1}{\sqrt{2}} = \frac{0.899}{\sqrt{2}}$$

$$|H_2(w_{c2})| = \frac{891}{991} * \frac{1}{\sqrt{2}} = \frac{0.899}{\sqrt{2}}$$

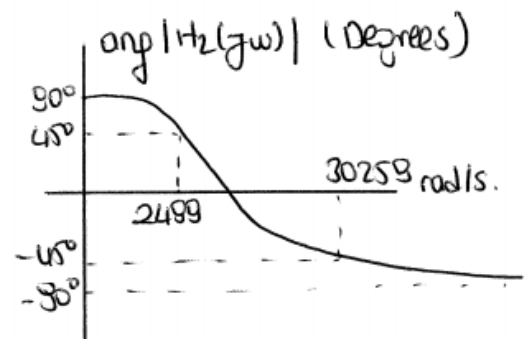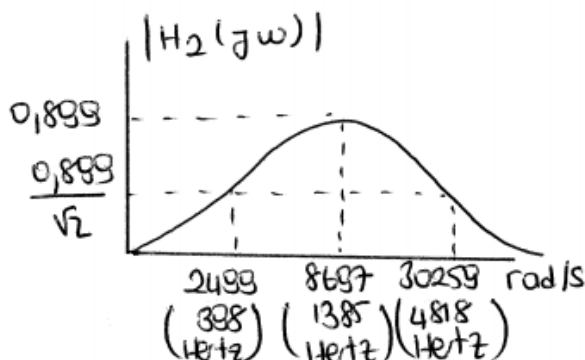

$$\Delta\omega = \omega_{c2} - \omega_{c1} = 27760\text{rad/sec}$$

$$|\omega_1 - \omega_2| = \text{bandwidth}$$


$$H(s) * H_1(s) = \frac{(33 * 10^3)}{\left(33s * 10^3 + \frac{10^8}{s}\right)} * \frac{2700}{2700 + 0.1s}$$

$$H(s) * H_1(s) = \frac{(5 * 33 * 27 * 10^5)}{(33s + 10^5)10^3(27000 + s)10^{-1}} \cong \frac{249575}{(s + 24696)(s + 3063)}$$

We can see that the gain the zeros and poles of two systems are so close to each other as seen allows.

3. $L=0.1\text{H}, \omega_o = 10\text{krad/sec}, V_i(t) = V\sin(\omega t)$

$$f_o = 1592\text{Hertz}$$

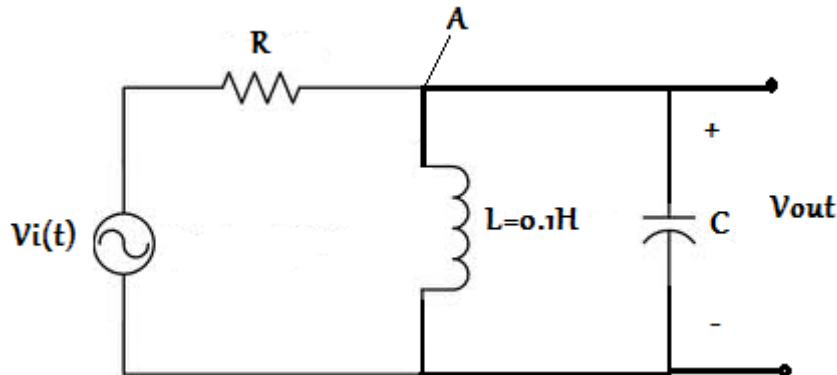

$$\frac{V_i - A}{R} = \frac{A}{j\omega * 0.1} + \frac{A}{\frac{1}{j\omega C}}$$

$$\frac{A}{V_i} = \frac{\omega}{\omega + j(\omega^2 CR - 10R)} = \frac{V_o(j\omega)}{V_i(j\omega)} = H(j\omega)$$

- a. $R = 3.3k\Omega$

To find the resonant angular frequency

$$\omega^2 CR - 10R = 0$$

$$C = \frac{10}{\omega_o^2} = \frac{10}{10^8} = 0.1\mu F$$

Value of C independent of R.

To find half-power frequency

$$\frac{\omega_c^2}{\omega_c^2 + (\omega_c^2 CR - 10R)^2} = \frac{1}{2}$$

$$\omega_c^4 - \left(2 + \frac{1}{3.3^2}\right) 10^8 \omega_c^2 + 10^{16} = 0$$

$$\omega_{c1} = 8599 \text{ rad/sec} \qquad f_1 = 1369 \text{ Hertz}$$

$$\omega_{c2} = 11625 \text{ rad/sec} \qquad f_2 = 1851 \text{ Hertz}$$

$$\Delta\omega = \omega_{c2} - \omega_{c1} = 3029 \text{ rad/sec}$$

$$Q = \frac{\omega_c}{\Delta\omega} = \frac{10000}{3029} = 3.3$$

a. $R = 10 \text{ k}\Omega, L = 0.1 \text{ H}, \omega_o = 10 \text{ krad/sec}, f_o = 1592 \text{ Hertz}$

$$C = 0.1 \mu\text{F}$$

Since it is independent of R.

To find half-power frequency

$$\frac{\omega_c^2}{\omega_c^2 + (\omega_c^2 CR - 10R)^2} = \frac{1}{2}$$

$$\omega_c^4 C^2 R^2 - 20\omega_c^2 CR^2 - \omega_c^2 + 100R^2 = 0$$

$$\omega_{c1} = 10510 \text{ rad/sec} \qquad f_1 = 1673 \text{ Hertz}$$

$$\omega_{c2} = 9517 \text{ rad/sec} \qquad f_2 = 1514 \text{ Hertz}$$


$$\Delta\omega = \omega_{c2} - \omega_{c1} = 998 \text{ rad/sec}$$

$$Q = \frac{\omega_c}{\Delta\omega} = \frac{10000}{998} \cong 10$$

$$H(j\omega) = \frac{\omega}{\omega + j(\omega^2 10^{-7} 10^4 - 10 * 10^4)}$$

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (\omega^2 10^{-3} - 10^5)^2}}$$
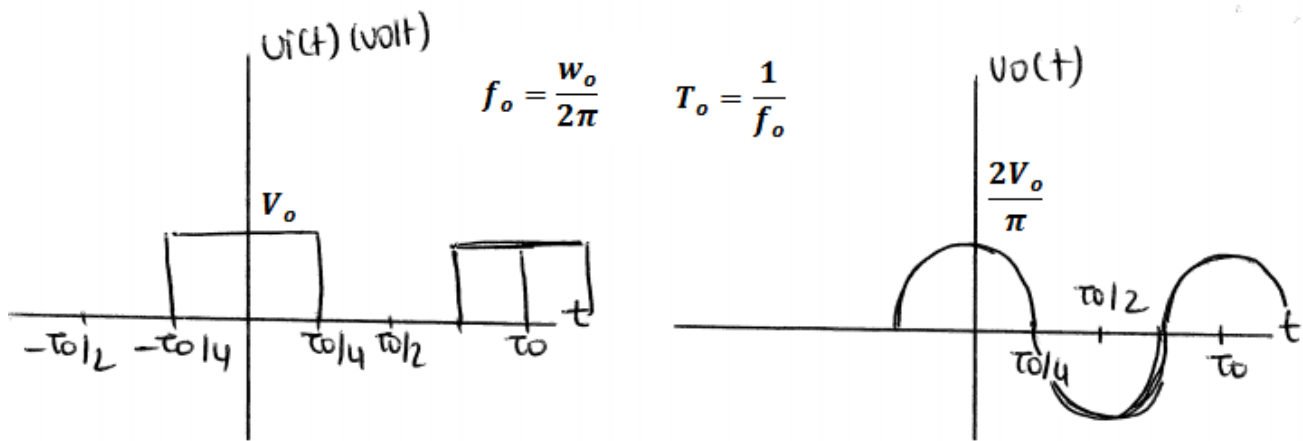
$$\arg(H(j\omega)) = \tan^{-1}\left(\frac{-\omega^2 10^{-3} - 10^5}{\omega}\right)$$



$$V_i(t) = V_o \left[\frac{1}{2} + \frac{2}{\pi} \cos(\omega_o t) - \frac{2}{3\pi} \cos(3\omega_o t) + \frac{2}{5\pi} \cos(5\omega_o t) - \dots \right]$$

Since the filter is a band-pass filter with critical frequency ω_o only the components of $V_i(t)$ with frequency ω_o passes. DC components and other frequencies dies out at the output.

4. In Preliminary work part 1, the filter is a high-pass filter.

In Preliminary work part 2a, the filter is a low-pass filter.

In Preliminary work part 2b, the filter is a band-pass filter.