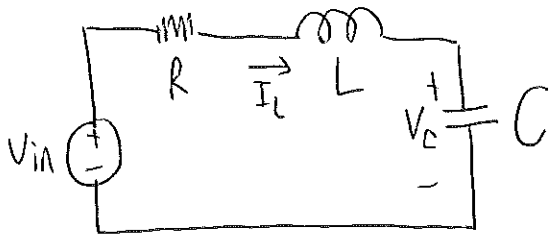


# Series RLC circuit

(1)



differential equations

$$\frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{1}{LC} V_C = \frac{1}{LC} V_{in}(t)$$

$$\frac{d^2 I_L}{dt^2} + \frac{R}{L} \frac{dI_L}{dt} + \frac{1}{LC} I_L = \frac{1}{L} \frac{dV_{in}(t)}{dt}$$

characteristic equation

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \text{let } 2\alpha = \frac{R}{L} \geq 0 \quad \omega_0^2 = \frac{1}{LC} > 0$$

$\alpha \rightarrow$  damping ratio  
 $\omega_0 \rightarrow$  resonant frequency

hence characteristic equation  $s^2 + 2\alpha s + \omega_0^2 = 0$

roots of characteristic equation  $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$  (natural frequencies)

(1) Assume  $V_{in}(t) = 1$  Volt

$$\frac{d^2 V_C}{dt^2} + 2\alpha \frac{dV_C}{dt} + \omega_0^2 V_C = \omega_0^2 \cdot 1 \rightarrow V_{cp} = 1 \quad V_C(t) = V_{cp} + V_{ch}$$

$$\frac{d^2 I_L}{dt^2} + 2\alpha \frac{dI_L}{dt} + \omega_0^2 I_L = \frac{1}{L} \cdot 0 \rightarrow I_{Lp} = 0 \quad I_L(t) = I_{Lp} + I_{Lch}$$

\* ~~Underdamped~~ case  $[\alpha > \omega_0]$   $\omega_d \triangleq \sqrt{\alpha^2 - \omega_0^2}$   $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$   
 Overdamped  $\frac{R}{2L} > \frac{1}{\sqrt{LC}}$   $\alpha > \sqrt{\alpha^2 - \omega_0^2} > 0 \rightarrow$  hence  $\rightarrow s_1 = -\alpha + \omega_d < 0$   
 $\rightarrow s_2 = -\alpha - \omega_d < 0$   
 (both natural frequencies are real and negative)

$$V_C(t) = 1 + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad \lim_{t \rightarrow \infty} V_C(t) = 1$$

$$I_L(t) = B_1 e^{s_1 t} + B_2 e^{s_2 t} \quad \lim_{t \rightarrow \infty} I_L(t) = 0$$

\* Critically damped case  $[\alpha = \omega_0]$   $\frac{R}{2L} = \frac{1}{\sqrt{LC}}$   $s_{1,2} = -\alpha$  (real, negative double root)  
 $-\alpha < 0$

$$V_C(t) = 1 + (A_1 + A_2 t) e^{-\alpha t}$$

$$I_L(t) = (B_1 + B_2 t) e^{-\alpha t}$$

(2)

\* Underdamped Case

$$\alpha < \omega_0$$

$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \rightarrow$  frequency (angular frequency) oscillations of damped natural frequencies

$$s_{1,2} = -\alpha \pm j\omega_d \text{ [complex roots]} \quad \text{Re}\{s_{1,2}\} < 0$$

$$V_c(t) = 1 + e^{-\alpha t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)]$$



$$I_c(t) = e^{-\alpha t} [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)]$$

\* Overdamped Case

$$V_c(0) = 0 \\ I_c(0) = 0 \Rightarrow$$



$$V_c(t) = 1 + \frac{s_2}{s_1 - s_2} e^{s_1 t} - \frac{s_1}{s_1 - s_2} e^{s_2 t}$$
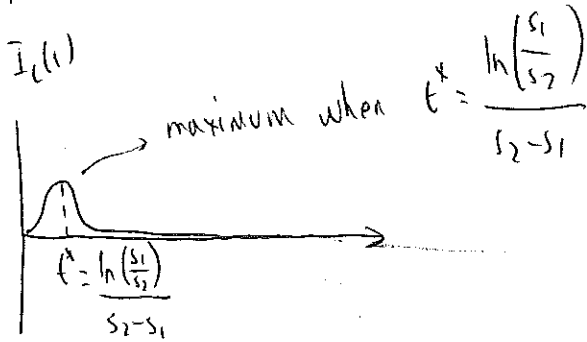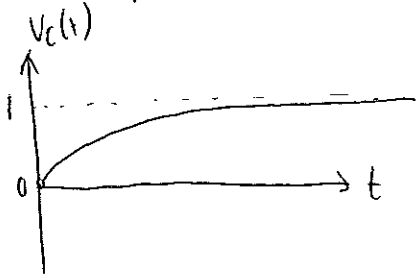
$$I_c(t) = \frac{C_1 s_2}{s_1 - s_2} e^{s_1 t} - \frac{C_1 s_1}{s_1 - s_2} e^{s_2 t}$$



\* Critically damped Case

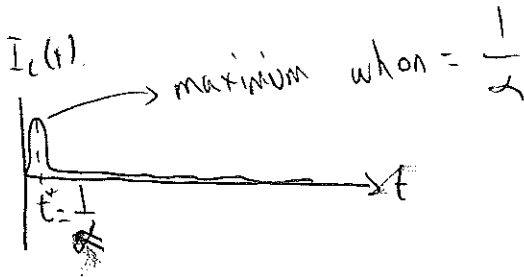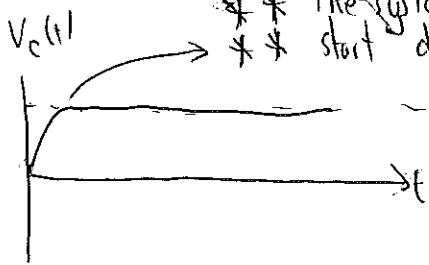\*\* The system will nearly start damped oscillations




$$V_c(0) = 0 \\ I_c(0) = 0 \\ V_c(t) = 1 + (-1 - \alpha t) e^{-\alpha t} \\ I_c(t) = \alpha^2 t e^{-\alpha t}$$

\* Underdamped case  $V_c(0)=0, I_L(0)=0$

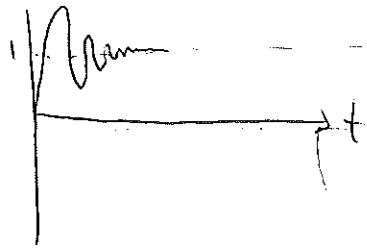(3)


$V_c(t)$

$$V_c(t) = 1 - e^{-\alpha t} \left[ \cos(\omega_d t) + \frac{\alpha}{\omega_d} \sin(\omega_d t) \right]$$



$$I_L(t) = C \frac{\omega_0}{\omega_d} \sin(\omega_d t) e^{-\alpha t}$$


$I_L(t)$

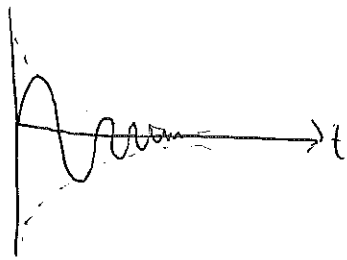

(2) Assume

$V_{in}(t)$

f = frequency of input

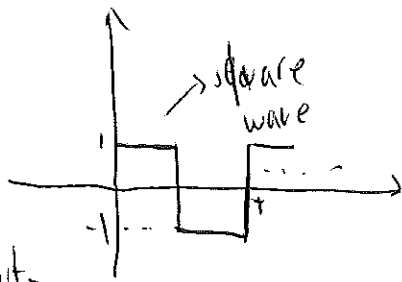

$T =$  period of input

If these assumptions are true the square wave can behave similar to a DC source

when  $Tk < t < \left(\frac{1+2k}{2}\right)T$   $V_{in}(t) = 1$   
 $k=0, \dots$   $V_{c,ss} = 1$   
 $I_{L,ss} = 0$

when  $\left(\frac{2k+1}{2}\right)T < t < (k+1)T$   $V_{in}(t) = -1$   
 $k=1, \dots$   $V_{c,ss} = -1$   
 $I_{L,ss} = 0$

Other assumptions (for steady-state conditions)

\*  $T \gg \tau_1, \tau_2$

$\tau_{1,2} \rightarrow$  time constants of the RLC circuit

\* For overdamped  $s = s_{1,2}$  (real negative)

$$\tau_1 = \frac{1}{|s_1|}, \tau_2 = \frac{1}{|s_2|} \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

\* For critically damped  $s_{1,2} = -\alpha$

$$\tau_1 = \frac{1}{|\alpha|}, \tau_2 = \frac{1}{|\alpha|}$$

\* For underdamped  $s_{1,2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$   
 $\text{Re}\{s_{1,2}\} = -\alpha \rightarrow$  determines exponential decay

hence  $\tau_1 = \frac{1}{|\alpha|}, \tau_2 = \frac{1}{|\alpha|}$


3

4

At steady-state conditions with square wave input


(when assumptions are satisfied)

\* Overdamped

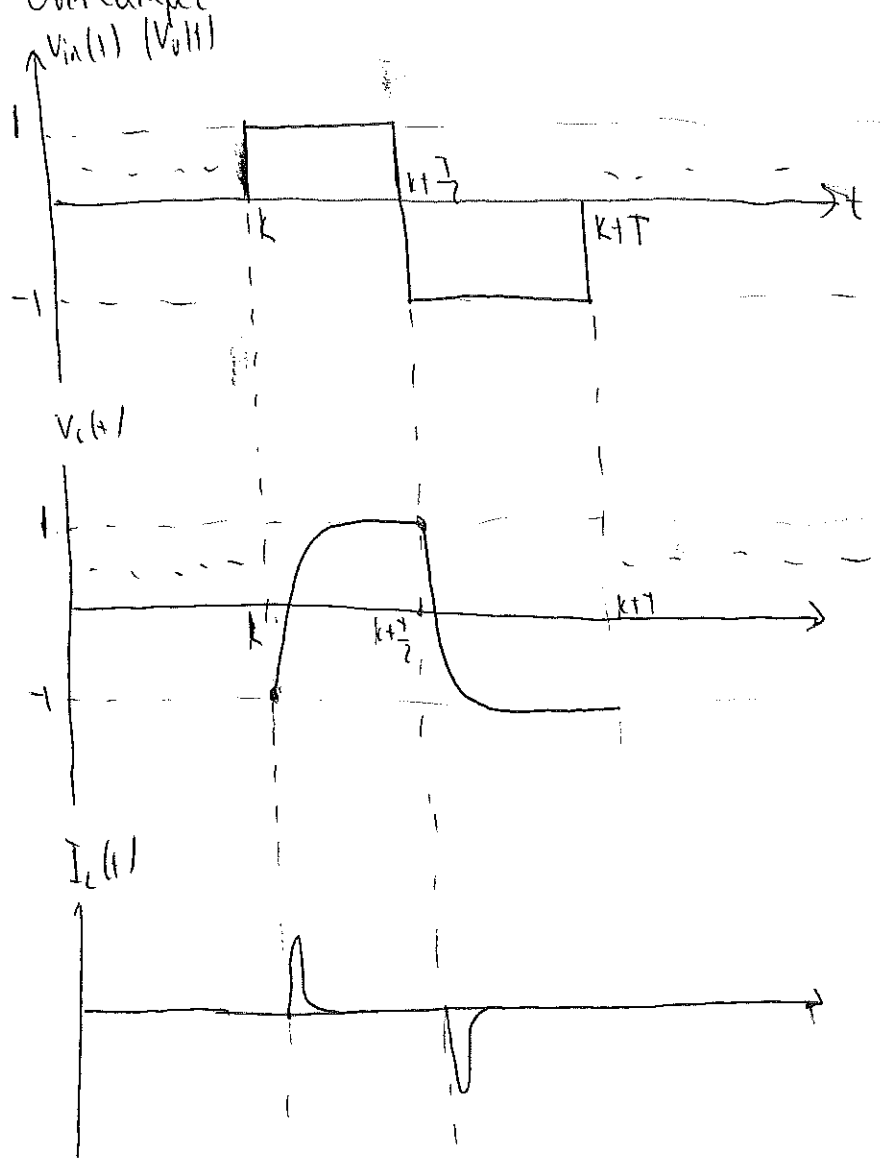

(5)

\* Critically damped

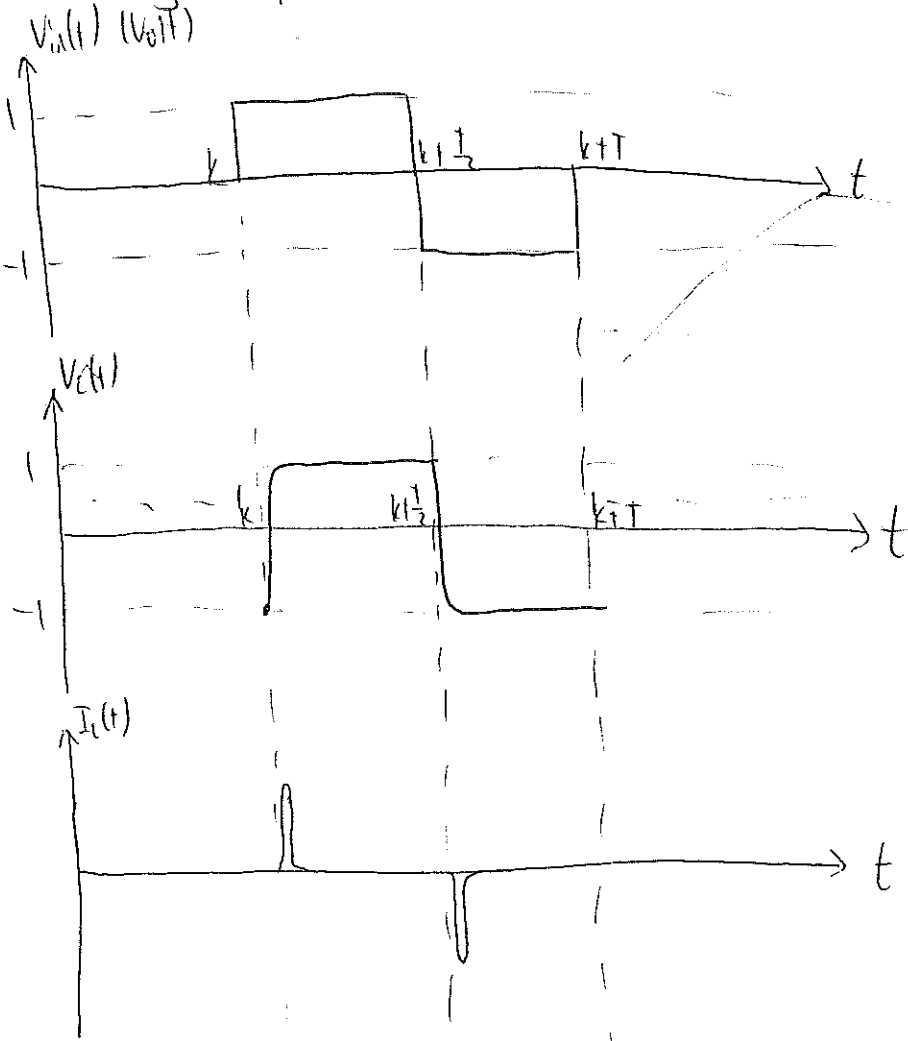

\* Underdamped

