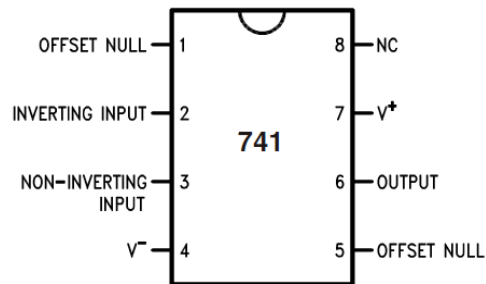



Ece 232

Lab1 supplementary notes:

LM741




1)

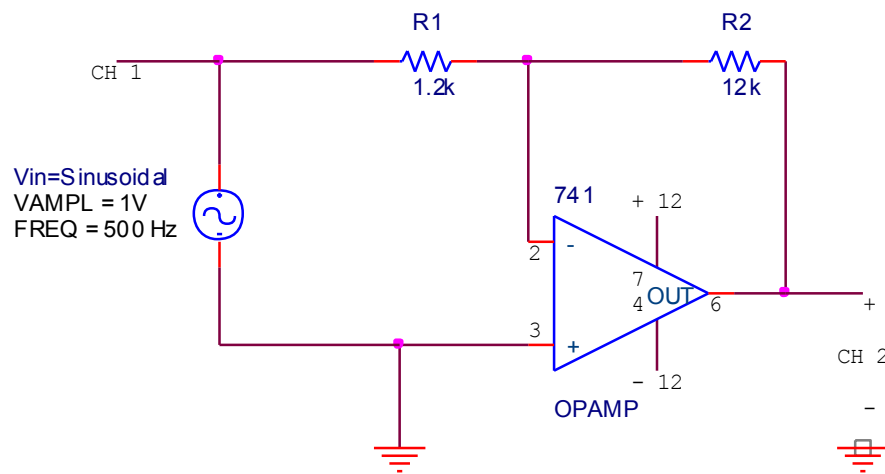


$$\frac{V_{in} - A}{R_1} = \frac{A - V_{out}}{R_2}, \quad A = 0 \text{ Volt}$$

$$V_{out} = -10V_{in}$$

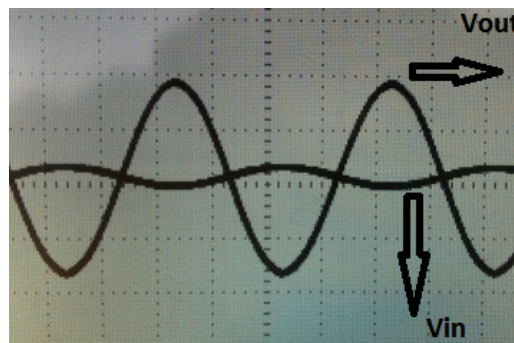if $V_{in}(t) = \sin(2\pi ft)$ then $V_{out}(t) = -10\sin(2\pi ft)$



2)

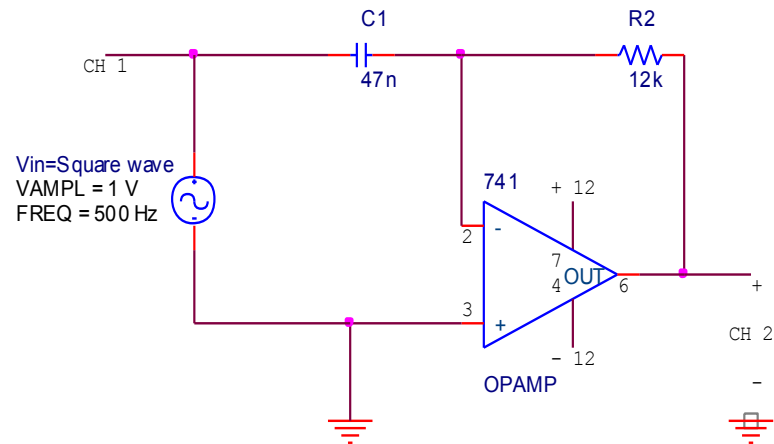

$$C_1 \frac{d(V_{in} - A)}{dt} = \frac{A - V_{out}}{R_2}$$


$$V_{out} = -C_1 R_2 \frac{dV_{in}}{dt}$$

$$C_1 R_2 = 564 \times 10^{-6}$$

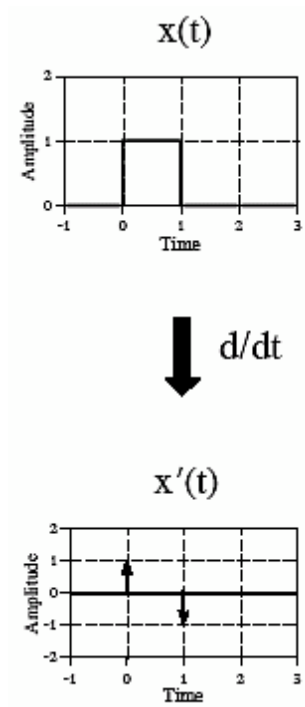a) If $V_{in}(t) = Sqr(ft)$ (square wave with frequency f and period T)

$$V_{in}(t) = \begin{cases} 1 \text{ Volt}, & 0 \leq t \leq \frac{T}{2} \\ -1 \text{ Volt}, & \frac{T}{2} \leq t \leq T \end{cases} \quad (\text{square wave})$$

$$V_{out}(t) = \begin{cases} -564 \times 10^{-6} \delta(t - n\frac{T}{2}), & n \text{ even} \\ -564 \times 10^{-6} \delta(t - n\frac{T}{2}), & n \text{ odd} \end{cases} \quad (\text{impulse train})$$



b) If $V_{in}(t) = Tri(ft)$ (triangular wave with frequency f and period T)


$$V_{in}(t) = \left\{ \begin{array}{ll} \frac{4}{T}t, & 0 \leq t \leq \frac{T}{4} \\ -\frac{4}{T}t + 2, & \frac{T}{4} \leq t \leq \frac{3T}{4} \\ \frac{4}{T}t - 4, & \frac{3T}{4} \leq t \leq T \end{array} \right\} \text{ (triangular wave)}$$

$$V_{out}(t) = \left\{ \begin{array}{ll} -564 \times 10^{-6} \frac{4}{T}, & 0 \leq t \leq \frac{T}{4} \\ 564 \times 10^{-6} \frac{4}{T}, & \frac{T}{4} \leq t \leq \frac{3T}{4} \\ -564 \times 10^{-6} \frac{4}{T}, & \frac{3T}{4} \leq t \leq T \end{array} \right\} \text{ (square wave)}$$

Example: If $f=500\text{Hz}$ and $T=2\text{ msec}$

$$V_{out}(t) = \begin{cases} -1.128 \text{ Volt}, & 0 \leq t \leq \frac{T}{4} \\ 1.128 \text{ Volt}, & \frac{T}{4} \leq t \leq \frac{3T}{4} \\ -1.128 \text{ Volt}, & \frac{3T}{4} \leq t \leq T \end{cases}$$

3.)

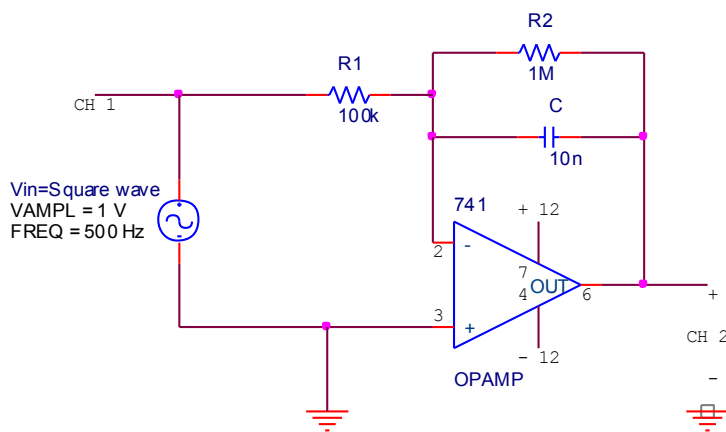

$$\frac{V_{in} - A}{R_1} = \frac{A - V_{out}}{R_2} + C \frac{d(A - V_{out})}{dt}$$

Since R_2 is very high the above equation can be written as,

$$\frac{V_{in} - A}{R_1} \cong C \frac{d(A - V_{out})}{dt}$$

Putting $A=0$ Volt we will have

$$\frac{dV_{out}}{dt} = -1000V_{in}$$

If the applied input is a square wave

$$V_{in}(t) = \begin{cases} 1 \text{ Volt}, & 0 \leq t \leq \frac{T}{2} \\ -1 \text{ Volt}, & \frac{T}{2} \leq t \leq T \end{cases} \quad \text{where } V_{in}(t) \text{ is periodic with period } T$$

$$V_{in} = 1 \text{ when } 0 \leq t \leq \frac{T}{2} \text{ hence}$$

$$\frac{dV_{out}}{dt} = -1000$$

$$V_{out}(t) = -1000t + X$$

Assuming $V_{out}(0) = V$ Volt and $f = 500$ Hz

$$V_{out}(t) = -1000t + V$$

$$V_{out}\left(\frac{T}{2}\right) = -1000\frac{T}{2} + V = -1000\frac{1}{500 \times 2} + V = V - 1$$

$$V_{in} = -1 \text{ when } \frac{T}{2} \leq t \leq T \text{ hence}$$

$$\frac{dV_{out}}{dt} = 1000$$

$$V_{out}(t) = 1000t + X$$


Knowing that $V_{out}(0.5T) = V - 1$ Volt and $f = 500$ Hz

$$V_{out}(t) = 1000t + V - 2$$

As the results


$$V_{out}(t) = \left\{ \begin{array}{ll} -1000t + V \text{ Volt}, & 0 \leq t \leq \frac{T}{2} \\ 1000t + V - 2 \text{ Volt}, & \frac{T}{2} \leq t \leq T \end{array} \right\} \text{ where } V_{in}(t) \text{ is periodic with period } T \text{ where}$$
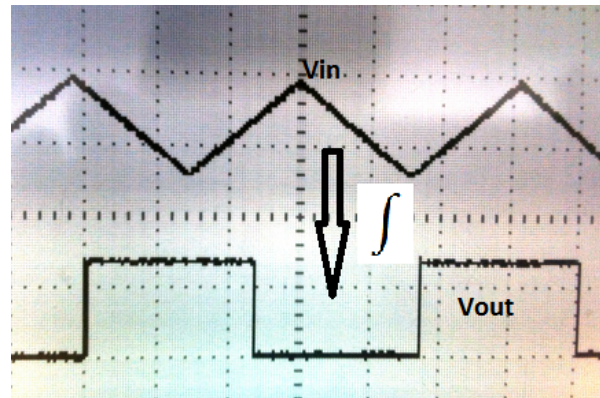
$$T = \frac{1}{f} = \frac{1}{500} = 2 \text{ msec}$$




Graphs


1) Inverting amplifier

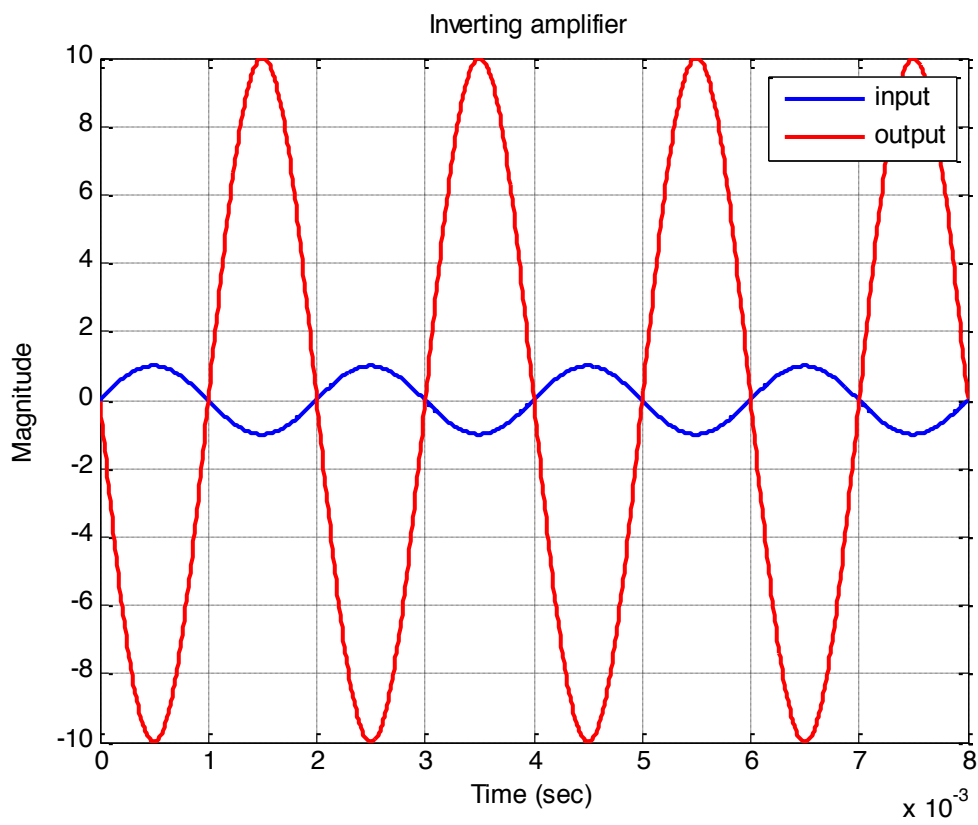

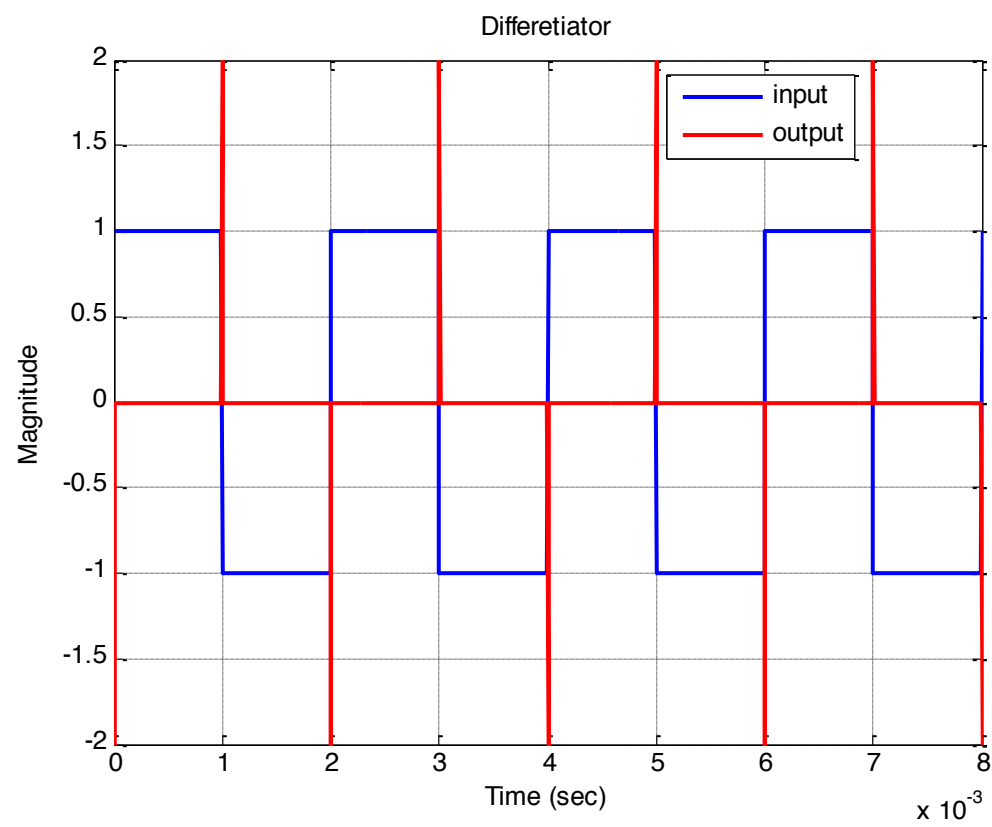2a) Differentiator (input is square wave)



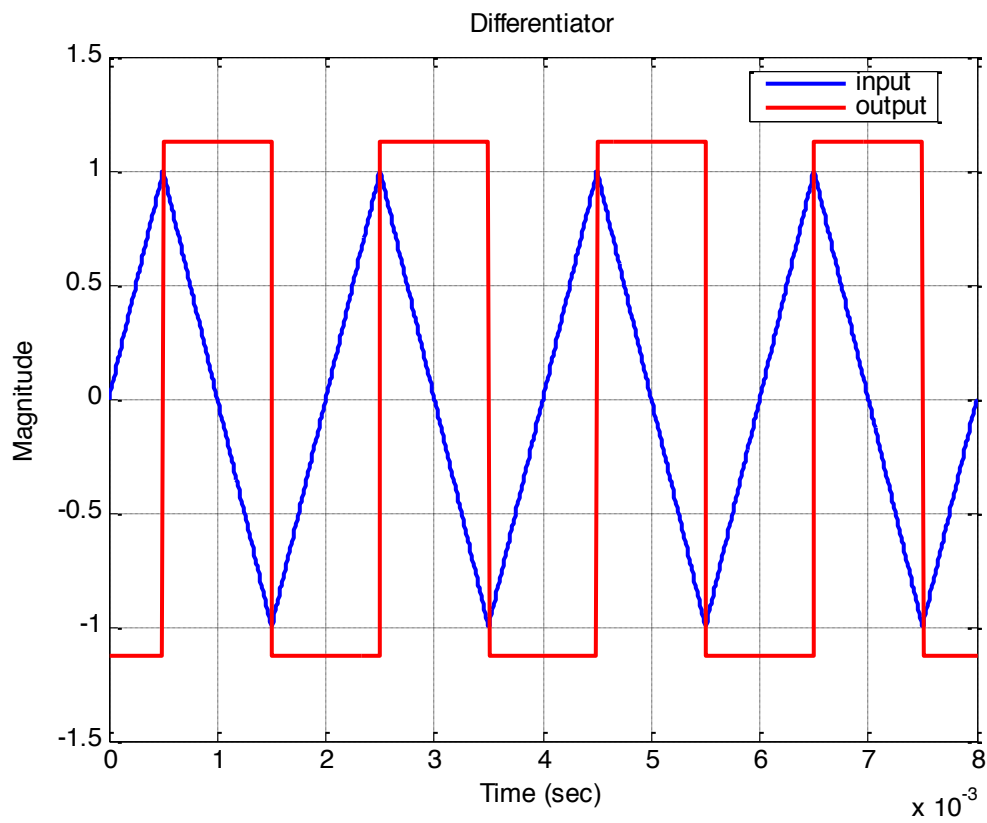2b) Differetiator (iput is triangular wave)



3) Integrator

